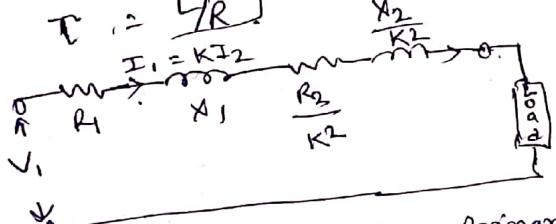


Representation of Power System Components.

- Three major components:- (1) Generation System. (2) Tx Sys (3) Dist Sys.
- 3- ϕ generation or supply as well as 3- ϕ Tx and networks are balanced. and therefore. So far as the calculation are concerned they can be treated as a single phase system for the analysis.
- In addition to the unbalanced supply or excitation, the 3- ϕ m/w is also unbalanced, their transformation into component quantities will not serve the purpose bcz even after transformation, the phasor quantities remain coupled. But such situation are not very common.
- For the development of fairly accurate model of the P.S networks, it is necessary that model reflects correctly the terminal behaviour of each component of the network for the purpose of study for which the model has been developed.
- Representation of synchronous generator for the purpose of transient stability studies is a constant voltage source behind proper reactance. The voltage source may be substituted by transient or steady state voltages.
- The current flowing in the syn gen just after occurrence of the three phase short ckt at its terminals is similar to the three phase short ckt at its terminal current that flows in an RL ckt upon which sudden ac voltage is applied. Hence the current will have both ac (i.e transient) & dc (i.e steady state) component as well as ~~dc~~ ac component which decays exponentially with time constant $T = \frac{L}{R}$.
- 

→ The 3- ϕ m/w consisting of transmission systems and also the distribution systems are assumed to be symmetrical or balanced.

- The performance of T/R line is governed by its four parameters - series R & L and shunt C & G.
- R → every conductor offers opposition to the flow of current
- L → the current carrying cond^r is surrounded by the magnetic lines of force.

$C \rightarrow$ cond^r carrying current forms a capacitor with earth.


$b \rightarrow$ due to flow of leakage currents over the surface of insulators especially during bad weather.

However, the conductance is normally neglected in the case of tx line calculation since leakages at normal freq are negligible.

\rightarrow Representation of Power System:

\rightarrow Single line diagram: main connections and components of the system components along with their data (such as output rating, voltage, resistance and reactance etc.).

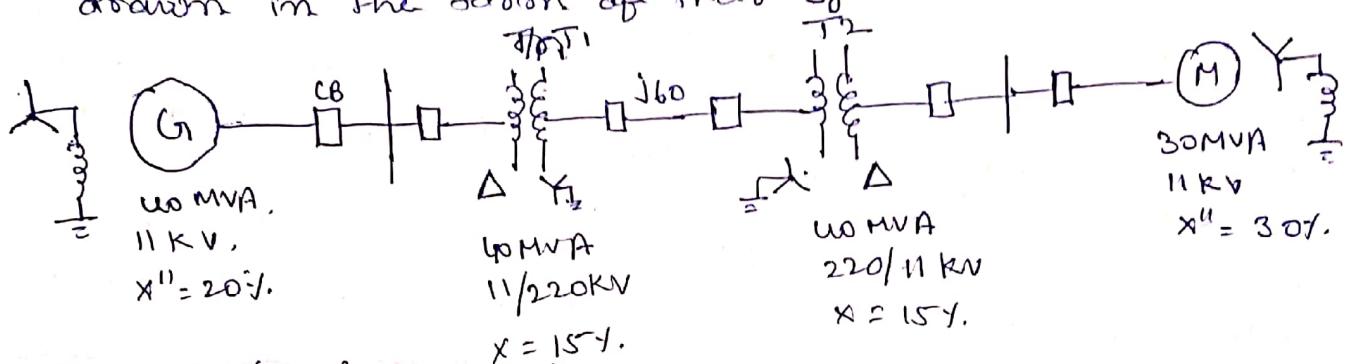
In single line diagram, the system components are usually drawn in the form of their symbols.



\rightarrow Any 3- ϕ sys consisting of gen, T/F, Tx line etc., can be solved as a single phase w/o composed of one of the three phases and a neutral return. If it is a balanced under normal operation. Many times, the components of the system are shown in a single line diagram omitting the neutral also.

\rightarrow Impedance diagram Representation of a power system.

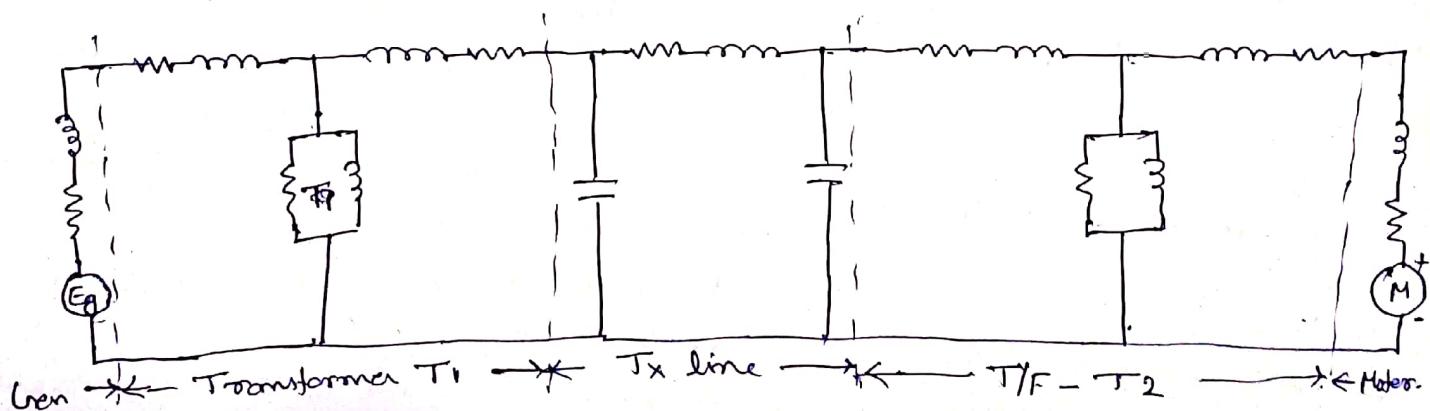
In impedance diagram each component is represented by its equivalent ckt. (Tx line by nominal π ckt).



\rightarrow Neutral earthing impedances do not appear in the diagram as balanced conditions are assumed.

- * i.e. impedance diagram known as positive sequence diagram since it is drawn for a balanced 3-ph system.
- * three separate (+ve, -ve & zero sequence) impedance diagrams are used in short ckt studies of unsymmetrical faults.

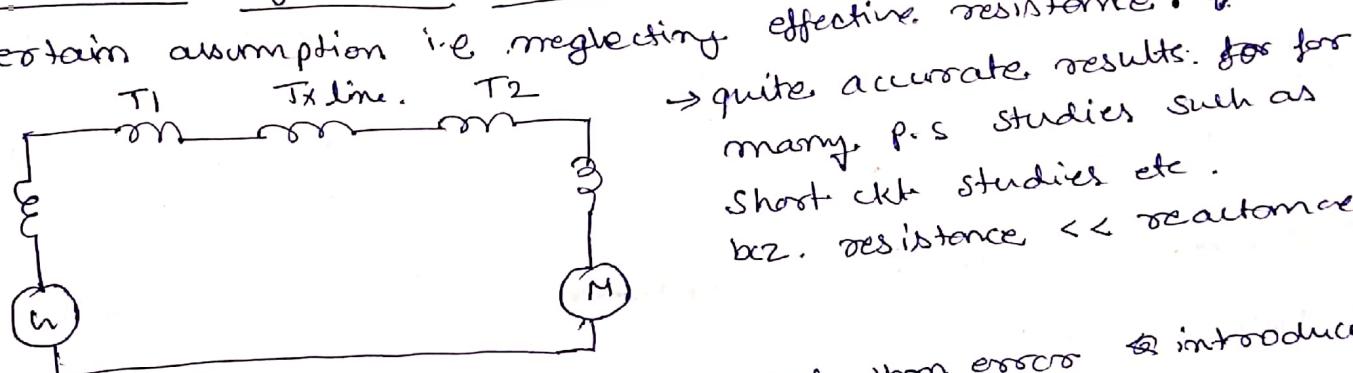→ Reactance diagram Representation of a P.S.



✓ Certain assumption i.e. neglecting effective resistance.

→ quite accurate results for many p.s studies such as short ckt studies etc.
bcz. resistance << reactance.

→ If the $R < \frac{1}{3}X$ and res neglected, then error is introduced.
will not be more than 5%.

If $R \leq \frac{1}{2}X$ then error 12% may be introduced.

By errors it is meant that calculation will result in values higher than is actually the case being obtained and in some cases, lead to purchase of protective gear with a higher rating than required.

→ Percentage Resistance and Reactance and Base kVA and KV.

$$\therefore R = \frac{IR}{V} \times 100.$$

I → full load current

V → rated voltage.

R → in ohm.

$$\therefore X = \frac{IX}{V} \times 100.$$

→ Base kVA: → If number of equipments such as gen/T.F. Tx line etc connected, it is difficult to compare $\propto R$ & $\propto X$ and their combined effect until and unless they are all referred to a common kVA. This common kVA which is arbitrary one is known as base kVA.

→ A base kVA may be chosen in the following manner.

(1) Equal to the kVA rating of the largest unit connected in the m/w.

(2) Equal to the sum of the kVA ratings of all the units connected in the m/w.

(3) Any arbitrary value.

For the calculation of short ckt current base MVA is to be taken into consideration.

→ Per unit method of representation

Pu value = The actual value of the quantity in any unit the base ref value, in the same unit.

→ Calculation are simplified.

→ By choosing suitable base KV's for the ckt's the per unit reactance remains the same, referred to either sides of T/F.

→ Provides a method of comparison.

$$\rightarrow \text{Base current } I_B = \frac{KVA_B}{KV_B}; \quad Z_B = \frac{V_B}{I_B} = \frac{V_B \times V_B}{I_B \times V_B}$$

$$= \frac{V_B^2 / 1000 \times 1000}{V_B I_B / 1000 \times 1000}$$

$$= \frac{(KV_B)^2 / 1000}{KV_A} \cancel{\times 1000}$$

$$= \frac{(KV_B)^2}{MVA_B}$$

→ If in the mhw there is no T/F present, the same base voltage is used throughout, but if the T/F are present, the rule is to change the base voltage in the proportion to the transformation ratio of the T/F. When T/F is reached.

$$I_{pu} = \frac{\text{Actual current}}{\text{Base current}} = I \cdot \frac{(KV)_B}{(KVA)_B}$$

$$Z_{pu} = Z \times \frac{MVA_B}{(KV_B)^2}$$

→ 3-φ system:

$$(Y) \rightarrow I_B = \frac{KV A_B}{\sqrt{3} KV_B}; \quad Z_B = \frac{(KV_B)^2}{MVA_B} = \frac{\left(\frac{KV_B}{\sqrt{3}}\right)^2}{MVA_B}$$

Z_B → some exp for 1-φ & 3-φ system.

$$Z_{pu\ new} = Z_{pu\ old} \times \frac{KVA_{new}}{KVA_{old}} \times \frac{(KV_{old})^2}{(KV_{new})^2}$$

① S-L-H. ② L-L-fault
③ L-L-H-fault ④

UNSYMMETRICAL FAULT ANALYSIS.

Condition before fault is $I_R = I_Y = I_B = 0$. \rightarrow unloaded condn

Step - I

At faulted bus K;

1st find I_{R0}, I_{R1}, I_{R2} .

Step - 2

For the known seq currents I_{R1}, I_{R2}, I_{R0} , the 3-ph currents at bus K

$$\begin{bmatrix} I_R \\ I_Y \\ I_B \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha^2 & \alpha \\ 1 & \alpha & \alpha^2 \end{bmatrix} \begin{bmatrix} I_{R0} \\ I_{R1} \\ I_{R2} \end{bmatrix}$$


Step - 3

The Seq Voltages = ?

$$V_{R1} = E - I_{R1} Z_1$$

$$V_{R2} = -I_{R2} Z_2$$

$$V_{R0} = -I_{R0} Z_0$$

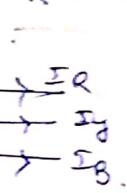

$$\begin{bmatrix} I_{R0} \\ I_{R1} \\ I_{R2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha^2 & \alpha \\ 1 & \alpha & \alpha^2 \end{bmatrix} \begin{bmatrix} I_R \\ I_Y \\ I_B \end{bmatrix}$$


Eq: 26

Step - 4

Finally determine the 3-ph voltages.

$$\begin{bmatrix} V_R \\ V_Y \\ V_B \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha^2 & \alpha \\ 1 & \alpha & \alpha^2 \end{bmatrix} \begin{bmatrix} V_{R0} \\ V_{R1} \\ V_{R2} \end{bmatrix}$$

S-L-H Fault

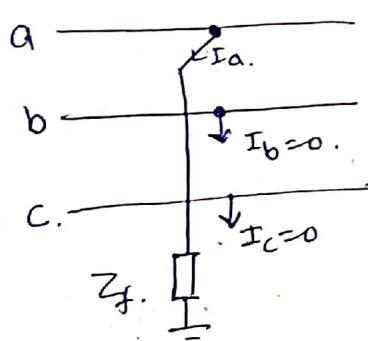

$$I_a = I_{f, LH}$$

$$I_b = I_c = 0$$

$$V_a = I_a Z_f$$

$$\begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha & \alpha^2 \\ 1 & \alpha^2 & \alpha \end{bmatrix} \begin{bmatrix} I_a \\ 0 \\ 0 \end{bmatrix}$$


$$\frac{\text{Step-1}}{I_{a1} = I_{a2} = I_{a0} = \frac{1}{3} I_a = \frac{1}{3} I_{f, LH}}$$

\hookrightarrow all seq N/W are in series.

$$I_{af} = 3 I_{a1} = 3 I_{f, LH}$$

$$\frac{\text{Step-2}}{I_a = 3 I_{a1} = I_{f, LH} = \frac{3 E_a}{(Z_1 + Z_2 + Z_3) + 3 Z_f}}$$

$$I_b = I_c = 0$$

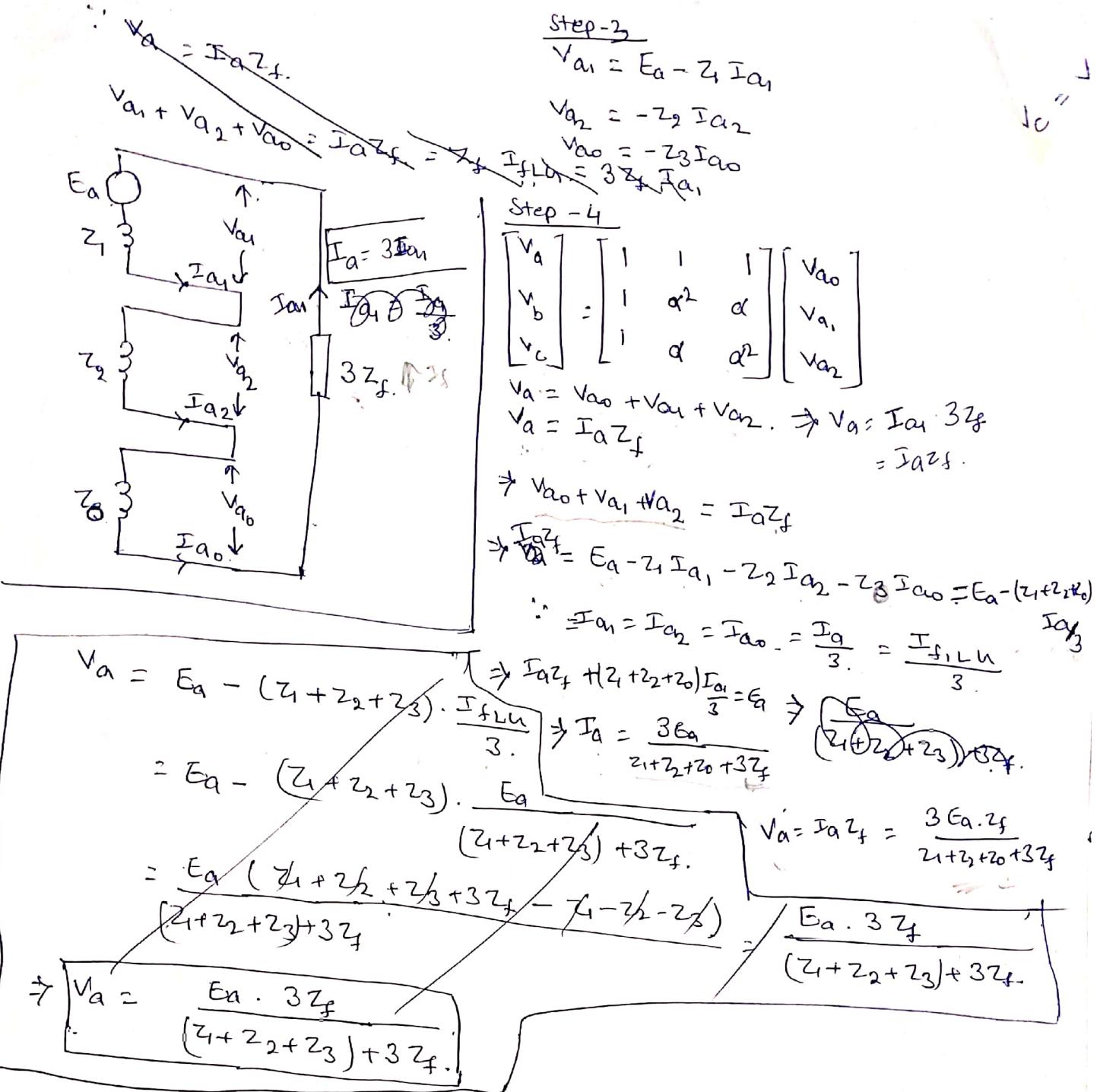

$V_b = V_{a_0} + \alpha^2 V_{a_1} + \alpha V_{a_2} = \alpha^2 \left(E_a - Z_1 \frac{I_a}{3} \right) + \alpha \left(-Z_2 \frac{I_a}{3} \right) + \left(-Z_0 \frac{I_a}{3} \right)$
 $= \alpha^2 E_a - \frac{I_a}{3} \left[\alpha^2 Z_1 + \alpha Z_2 + Z_0 \right]$
 $= \alpha^2 E_a - \frac{E_a (\alpha^2 Z_1 + \alpha Z_2 + Z_0)}{Z_1 + Z_2 + Z_0 + 3Z_f}$
 $= \frac{E_a [\alpha^2 (Z_1 + Z_2 + Z_0 + 3Z_f) - \alpha^2 Z_1 - \alpha Z_2 - Z_0]}{(Z_1 + Z_2 + Z_0) + 3Z_f}$
 $V_b = \frac{E_a [Z_2 (\alpha^2 - \alpha) + Z_0 (\alpha^2 - 1) + 3Z_f]}{(Z_1 + Z_2 + Z_0) + 3Z_f}$


(2)

$$\begin{aligned}
 V_C &= V_{a_0} + \alpha V_{a_1} + \alpha^2 V_{a_2} \\
 &= \alpha V_{a_1} + \alpha^2 V_{a_2} + V_{a_0} \\
 &= \alpha \left[E_a - Z_1 \frac{I_a}{3} \right] + \alpha^2 \left(-Z_2 \frac{I_a}{3} \right) + \left(-Z_0 \frac{I_{a_0}}{3} \right) \\
 &= \alpha E_a - \frac{I_a}{3} \left[\alpha Z_1 + \alpha^2 Z_2 + Z_0 \right] \\
 &= \alpha E_a - \frac{E_a (\alpha Z_1 + \alpha^2 Z_2 + Z_0)}{Z_1 + Z_2 + Z_0 + 3 Z_f} \\
 &= \frac{E_a [\alpha (Z_1 + Z_2 + Z_0 + 3 Z_f) - \alpha Z_1 - \alpha^2 Z_2 - Z_0]}{Z_1 + Z_2 + Z_0 + 3 Z_f} \\
 &\approx \frac{E_a [Z_2 (\alpha - \alpha^2) + Z_0 (\alpha - 1) + 3 \alpha Z_f]}{Z_1 + Z_2 + Z_0 + 3 Z_f}.
 \end{aligned}$$

\Rightarrow For. S-L-n fault.

$I_{a_1} = I_{a_2} = I_{a_0} = \frac{I_a}{3} = \frac{1}{3} I_{f.LN}$	Sequence currents
$I_a = 3 I_{a_1} = I_{f.LN} = \frac{3 E_a}{Z_1 + Z_2 + Z_3 + 3 Z_f}$	Phase current.
$I_b = I_c = 0$	
$V_{a_1} = E_a - Z_1 I_{a_1}$ $V_{a_2} = -Z_2 I_{a_2}$ $V_{a_0} = -Z_3 I_{a_0}$	Sequence voltages
$V_a = \frac{E_a - 3 Z_f}{(Z_1 + Z_2 + Z_3) + 3 Z_f}$	
$V_b = \frac{E_a [Z_2 (\alpha^2 - \alpha) + Z_0 (\alpha^2 - 1) + 3 \alpha^2 Z_f]}{Z_1 + Z_2 + Z_0 + 3 Z_f}$	Phase voltages
$V_c = \frac{E_a [Z_2 (\alpha - \alpha^2) + Z_0 (\alpha - 1) + 3 \alpha Z_f]}{Z_1 + Z_2 + Z_0 + 3 Z_f}$	

L-L-B Fault :-

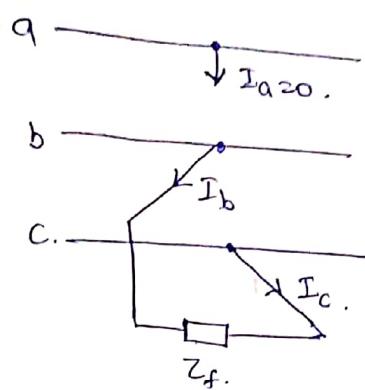

$$I_a = 0, \quad I_b = I_c = I_{f,LL}.$$

$$V_b - V_c = I_b Z_f. \Rightarrow V_c = V_b - I_b Z_f.$$

$$\begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha & \alpha^2 \\ 1 & \alpha^2 & \alpha \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 0 \\ I_b \\ -I_b \end{bmatrix}$$

$$I_{a0} = \frac{1}{3}[I_b - I_b] = 0.$$


$$I_{a1} = \frac{1}{3}[0 + \alpha I_b - \alpha^2 I_b] = \frac{1}{3} I_b (\alpha - \alpha^2).$$

$$I_{a2} = \frac{1}{3}[0 + \alpha^2 I_b - \alpha I_b] = \frac{1}{3} I_b (\alpha^2 - \alpha) = -I_{a1}$$

$$\begin{aligned} & \alpha^2 - \alpha \\ &= \alpha(\alpha - 1) \\ &= (-0.5 + j0.88) \times \\ & \quad (-0.5 + j0.88 - 1) \\ &= (-0.5 + j0.88) \times \\ & \quad (-1.5 + j0.88) \\ &= 0.00044 \times j1.732 \\ &= -j\sqrt{3}. \end{aligned}$$

Step - 1 \Rightarrow $\boxed{\begin{array}{l} I_{a0} = 0 \\ I_{a2} = -I_{a1} = \frac{1}{3} I_b (\alpha^2 - \alpha) \end{array}} = \frac{1}{3} I_{f,LL} \cdot (-j\sqrt{3}).$
seq. currents.

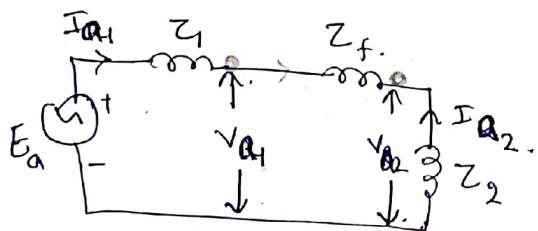Step - 2 \Rightarrow $\boxed{I_a = 0; I_b = I_c} \rightarrow$ phase currents.



$I_{a0} = 0$ so zero seq
nw is unconnected.

$$|I_{f,LL}| = \frac{\sqrt{3} E_a}{Z_1 + Z_2 + Z_f}$$

$$\begin{aligned} I_{a2} &= -I_{a1} = \frac{1}{\sqrt{3}} I_{f,LL} (-j\sqrt{3}) = -\frac{I_{f,LL}}{j\sqrt{3}} \\ &= -\frac{E_a}{Z_1 + Z_2 + Z_f}. \end{aligned}$$

$$\Rightarrow I_{f,LL} = j\sqrt{3} I_{a2} = j\sqrt{3} I_{a1} = -j\sqrt{3} \frac{E_a}{Z_1 + Z_2 + Z_f}$$

$$\Rightarrow \boxed{I_{f,LL} = -\frac{j\sqrt{3} E_a}{Z_1 + Z_2 + Z_f} = I_{a2} = -I_{a1}}$$

Step - 3

$$V_{a1} = E_a - I_{a1} Z_1$$

from
ext.

$$V_{a2} = -I_{a2} Z_2$$

$$V_{a1} - V_{a2} = I_{a1} Z_f$$

$$\text{or. } \begin{bmatrix} V_{a0} \\ V_{a1} \\ V_{a2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha & \alpha^2 \\ 1 & \alpha^2 & \alpha \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} = \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} - I_{f,LL} Z_f$$

(3)

$$V_{A_0} = \frac{1}{2} [V_A + V_B + V_B - Z_f I_b] = \frac{1}{2} [V_A + 2V_B - Z_f I_b]$$

$$V_{A_1} = \frac{1}{2} [V_A + \alpha V_B + \alpha^2 (V_B - Z_f I_b)]$$

$$= \frac{1}{2} [V_A + V_B (\alpha + \alpha^2) - \alpha^2 Z_f I_b]$$

$$\Rightarrow 3V_{A_1} = V_A + V_B (\alpha + \alpha^2) - \alpha^2 Z_f I_b. \quad \text{--- (1)}$$

$$\text{Similarly, } 3V_{A_2} = V_A + V_B (\alpha + \alpha^2) V_B - \alpha Z_f I_b. \quad \text{--- (2)}$$

from (1) - (2).

$$3V_{A_1} - 3V_{A_2} = Z_f I_b (\alpha - \alpha^2) = +j\sqrt{3} Z_f I_b.$$

$$\Rightarrow V_{A_1} - V_{A_2} = -\frac{Z_f I_b}{j\sqrt{3}}$$

$$\therefore I_b = -\frac{1}{3} Z_f I_b (\alpha^2 - \alpha) = -\frac{1}{2} (-j\sqrt{3}) I_b = -j\frac{I_b}{\sqrt{3}}$$

$$\Rightarrow I_b = -j\sqrt{3} I_a$$

$$\text{Now, } V_{A_1} - V_{A_2} = -\frac{Z_f I_b}{j\sqrt{3}} = -\frac{Z_f}{j\sqrt{3}} \times -j\sqrt{3} I_a = Z_f I_a$$


$$\Rightarrow \boxed{V_{A_1} - V_{A_2} = Z_f I_a}$$

Now from seq currents & seq voltage eqⁿ. +ve & -ve seq. are in parallel connection and. $\because I_{A0} = 0$ so zero seq m/s is unconnected.

$$\begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha^2 & \alpha \\ 1 & \alpha & \alpha^2 \end{bmatrix} \begin{bmatrix} V_{A_0} \\ V_{A_1} \\ V_{A_2} \end{bmatrix} = V_{A_0} + Z_f I_a$$

$$V_A = V_{A_0} + V_{A_1} + V_{A_2} = V_{A_0} + V_{A_1} + V_{A_1} - Z_f I_a = V_{A_0} + 2V_{A_1} - Z_f I_a$$

L-L-Ln Fault

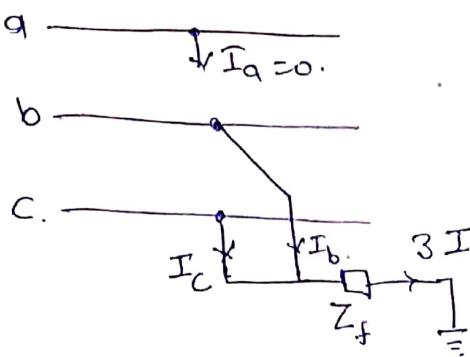

$$I_a = 0.$$

$$V_b = V_c = Z_f (I_b + I_c) = 3 Z_f I_{f,LLN}.$$

$$I_{f,LLN} = \frac{I_b + I_c}{3}$$

$$\begin{bmatrix} V_{a_0} \\ V_{a_1} \\ V_{a_2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha & \alpha^2 \\ 1 & \alpha^2 & \alpha \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix}$$

$$V_{a_0} = \frac{1}{3} [V_a + V_b + V_c] = \frac{1}{3} (V_a + 2V_b). \quad \text{--- (1)}$$

$$V_{a_1} = \frac{1}{3} [V_a + \alpha V_b + \alpha^2 V_c] = \frac{1}{3} [V_a + (\alpha + \alpha^2) V_b].$$

$$V_{a_2} = \frac{1}{3} [V_a + \alpha^2 V_b + \alpha V_c] = \frac{1}{3} [V_a + (\alpha + \alpha^2) V_b]$$

$$\Rightarrow V_{a_1} = V_{a_2} = \frac{1}{3} [V_a + V_b(\alpha + \alpha^2)]. \quad \text{--- (2)}$$

means +ve & -ve seq. m/w are in parallel.



Now,

$$\begin{aligned} V_{a_0} - V_{a_1} &= \frac{1}{3} (V_a + 2V_b) - \frac{1}{3} [V_a + V_b(\alpha + \alpha^2)] \\ &= \frac{1}{3} [V_a + 2V_b - V_a - V_b(\alpha + \alpha^2)] \\ &= \frac{1}{3} V_b (2 - \alpha - \alpha^2) = V_b = 3 Z_f I_{a_0}. \end{aligned}$$

$$\begin{aligned} 2 - \alpha - \alpha^2 - 1 + 1 \\ = 2 - (\alpha + \alpha^2 + 1) + 1 \\ = 3 - (1 + \alpha + \alpha^2) \\ = 3 - 0 = 3. \end{aligned}$$

$$\Rightarrow V_{a_0} = V_{a_1} + 3 Z_f I_{a_0}.$$

$$= V_{a_2} + 3 Z_f I_{a_0}.$$

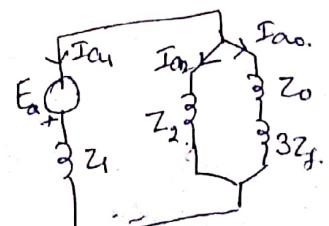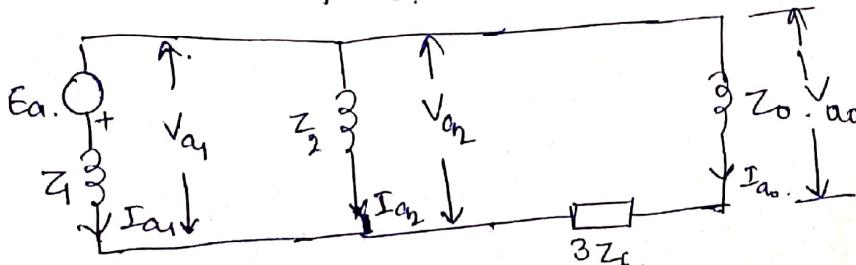

$$I_{a_1} = \frac{E_a}{z_1 + z_2 / (z_0 + 3z_f)} = \frac{E_a}{z_1 + z_2 (z_0 + 3z_f) / (z_2 + z_0 + 3z_f)}$$

$$I_{a_2} = -I_{a_1} \cdot \frac{z_0 + 3z_f}{z_2 + z_0 + 3z_f}$$

$$I_{a_0} = -I_{a_1} \cdot \frac{z_2}{z_2 + z_0 + 3z_f}$$

$$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha^2 & \alpha \\ 1 & \alpha & \alpha^2 \end{bmatrix} \begin{bmatrix} I_{a_0} \\ I_{a_1} \\ I_{a_2} \end{bmatrix}$$

$$\begin{aligned} & \frac{E_a \cdot (z_2 + z_0 + 3z_f)}{z_1 (z_2 + z_0 + 3z_f) + z_2 (z_0 + 3z_f)} \\ &= \frac{\cancel{E_a (z_2 + z_0 + 3z_f)}}{\cancel{z_1 (z_2 + z_0 + 3z_f) + z_2 (z_0 + 3z_f)}} \end{aligned}$$

$$I_a = I_{a_0} + I_{a_1} + I_{a_2} = -I_{a_1} \frac{z_2}{z_2 + z_0 + 3z_f} - I_{a_1} \frac{z_0 + 3z_f}{z_2 + z_0 + 3z_f} + I_{a_0}$$

$$= \frac{-I_{a_1}}{z_2 + z_0 + 3z_f} (z_2 + z_0 + 3z_f) + I_{a_2} = I_{a_2} - I_{a_1}$$

$$I_b = I_{a_0} + \alpha^2 I_{a_1} + \alpha I_{a_2}$$

$$I_c = I_{a_0} + \alpha I_{a_1} + \alpha^2 I_{a_2}$$

PER UNIT SYSTEM

(1)

- A per unit method uses Per unit values.
- A per unit value is a unit less quantities.
- P.U Value =
$$\frac{\text{Actual value in some unit}}{\text{Base or ref value in same units}}$$
- P.U value $\times 100 = \%$ value.

Advantages of P.U method.

- It Simplifies Power System calculations.
- It avoids the discontinuities problem posed by the presence of T/F.

Selection of Base Values.

- We only select base values from power, voltage, current and impedance.

$$\rightarrow \text{Base Power} = \begin{cases} \text{KVA}_b \\ \text{MVA}_b \end{cases} ; \quad \text{Base Current (I}_b \text{ in Amp)} = \begin{cases} \frac{\text{KVA}_b}{\text{KV}_b} \\ \frac{\text{MVA} \times 1000}{\text{KV}_b} \end{cases}$$

$$\text{Base Voltage} = \text{KV}_b ; \quad \text{Base Impedance (Z}_b \text{ in } \Omega) = \frac{\text{KV}_b^2}{\text{MVA}_b} \text{ or } \frac{\text{KV}_b^2}{\text{KVA}_b / 1000}$$

- The base Power and base voltage always selected and other two (I_b, Z_b) is derived.
- Dimension of actual and base value must be match.

3-Φ System

Base quantities are 3-Φ quantities i-e 3-Φ Power and line voltages.

$$\text{Base Power} = \text{KVA}_b, 3\Phi, \text{MVA}_b, 3\Phi$$

$$\text{Base Voltage} = \text{KV}_b, \text{line.}$$

- 3-Φ system always work on single phase basis bcz phases are symmetrical after that ems is converted to 3-Φ quantities.

- we assume many thing e.g. 3Φ system is balanced and star connected. Short Tx line is in star connected, anticlockwise dirⁿ is +ve.

ratios are in 11 kV, 33 kV, 132 kV -- there is no reason only conversion.
$$\sqrt{3} V_p I_p \text{ (a.u)} = 3 \cdot \frac{1}{\sqrt{3}} I_L \text{ (a.u)}$$

$$\rightarrow P_{3\Phi} = \sqrt{3} V_L I_L \cos \phi$$

$$Z_b = \frac{MVA_{b,3\phi}/3}{\frac{KV_b}{\sqrt{3}} \times 1000} \text{ Amp. } = \frac{KV_{b,3\phi}}{\sqrt{3} \cdot KV_{b,\text{line}}}.$$



$$Z_{b,3\phi} = \frac{(KV_{b,\text{line}})^2}{MVA_{b,3\phi}} = \frac{\left(\frac{KV_{b,1}/\sqrt{3}}{\sqrt{3}}\right)^2}{\frac{MVA_{b,3\phi}}{3}} = \frac{KV_b^2}{MVA_b} = Z_{b,1\phi}$$

$$\Rightarrow Z_{b,3\phi} = Z_{b,1\phi}.$$

→ The base values selected in 3-φ system is pure 3-φ quantities.


→ A single line diagram representation of P.S indicates that the P.S is 3-φ, ~~so~~ balanced load. So, test analysis is for 1-φ basis for 3-φ system.

→ A P.S m/w. containing per unit impedances represents 1-φ m/w.

$$\rightarrow Z_{pu,\text{new}} = Z_{pu,\text{old}} \left(\frac{KV_{b,\text{old}}}{KV_{b,\text{new}}} \right)^2 \times \frac{MVA_{b,\text{new}}}{MVA_{b,\text{old}}}$$

→ When T/F is present in the m/w.

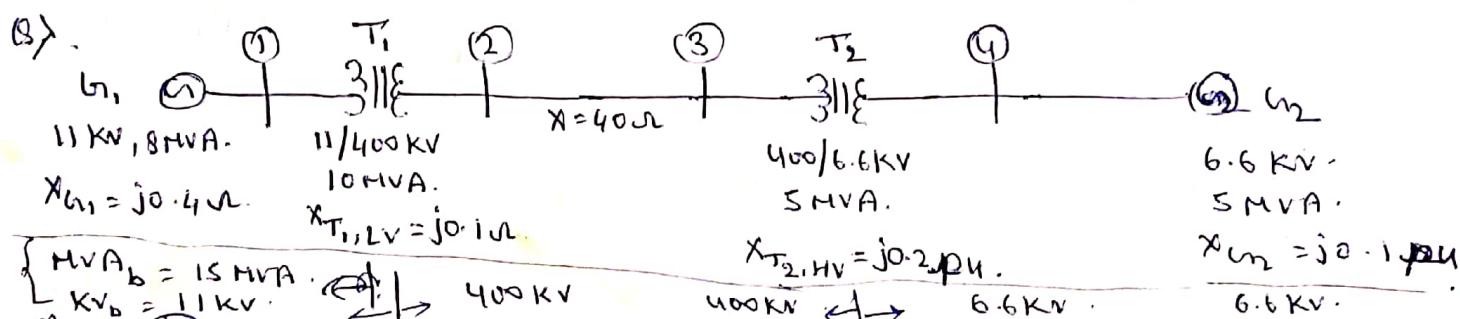↳ two sets of base values must be selected per either side of T/F.
or a common base value for entire m/w. } & their ratio
must be equal to.
Transformation ratio
of actual T/F.



$$\text{Solt: } - \quad (b_1) \quad V_{un} = \frac{11 \text{ kV}}{11 \text{ kV}} = 1 \text{ pu.}$$

$$X_{un,b} = \frac{j0.4 \cdot (11 \text{ kV})^2}{15} = 8.06.$$

$$X_{un} (\text{pu}) = \frac{j0.4}{8.06} = j0.049 \text{ pu.}$$

$$(b_2) \quad V_{un} = \frac{6.6 \text{ kV}}{6.6 \text{ kV}} = 1 \text{ pu.}$$

$$X_{un2,b} = \frac{(6.6)^2}{15} = 2.904$$

or,

$$X_{un2,\text{new}} (\text{pu}) = j0.1 \times \frac{(6.6)^2}{5} \times \frac{15}{5} \\ = j0.3 \text{ pu.}$$

$$X_{un2} (\text{pu}) = j0.1 \text{ pu on base of } 6.6 \text{ kV &} 5 \text{ MVA.}$$

$$= X_{un2} \frac{5}{(6.6)^2} \Rightarrow X_{un2} = j0$$

$$X_{un2} = j0.1 \times \frac{(6.6)^2}{5} = j0.871$$

$$X_{un2} (\text{pu new}) = \frac{j0.871}{2.904} = j0.3 \text{ pu.}$$

$$\textcircled{T}_1 \quad Y_{T_1, LV} = j0.1 \text{ u}.$$

$$X_{T_1, HV} = j0.1 \text{ u} \times \left(\frac{400}{11}\right)^2 \\ = j132.2 \text{ u.}$$

$$X_{T_1, (\text{pu})} \Rightarrow \frac{j0.1}{8.06} = j0.012 \text{ pu. (Primary)} \\ \rightarrow \frac{j132.2}{10666.6 \text{ u}} = j0.12 \text{ pu. (Secondary)} \quad b = \frac{(kV)^2}{mVA} = \frac{400^2}{15} \\ = 10666.67.$$

pu values of T/F whether it is on LV & HV side is same.


$$\frac{I_2}{I_1} = \frac{V_1}{V_2} = a \Rightarrow Z_1 = \frac{V_1}{I_1} = \frac{aV_2}{I_2/a} = a^2 \cdot \frac{V_2}{I_2} \\ \Rightarrow V_1 = a^2 Z_2 \\ \Rightarrow Z_2 = \frac{1}{a^2} Z_1$$

$$\textcircled{T}_2 \quad X_{T_2, HV} = j0.2 \text{ pu.}$$

$$X_{T_2, HV \text{ (new)}} = j0.2 \times \left(\frac{kV_{\text{old}}}{kV_{\text{new}}}\right)^2 \times \left(\frac{MVA_{\text{old}}}{MVA_{\text{new}}}\right) = j0.2 \times \left(\frac{400}{400}\right)^2 \times \frac{15}{5} = j0.6 \text{ pu.} \\ = j0.2 \times \left(\frac{6.6}{6.6}\right)^2 \times \frac{15}{5} = j0.6 \text{ pu.}$$

Tx line. (on HV side of T_1/T_2) .
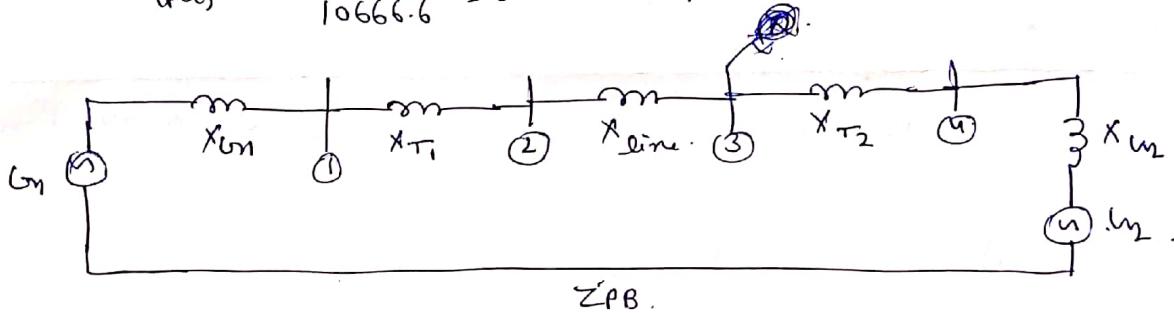
$$X_{\text{line (pu)}} = j \frac{340}{10666.6} = j0.00375 \text{ pu.}$$



per unit equivalent reactance diagram.

→ A base kVA may be chosen in the following manner.


- ① Equal to the kVA rating of the largest unit connected in the m/w.
- ② Equal to the sum of the kVA ratings of all the units connected in the m/w.
- ③ Any arbitrary value.

- Three major components in P.S representation - Generation, Tx & distribution system.
- 3- ϕ supply & Tx are balanced, so study on the basis of 1- ϕ .
- In case of unbalanced sys, study on the basis of component.
- Sym gen for transient study represented by const v source, with series reactance, v_{source} may be subtransient or steady state.
- The current flowing in the sym gen just after occurrence of the three phase short ckt at its terminal is similar to current that flows in an RL ckt upon which sudden ac voltage is applied. Hence current will have both both dc (steady state) component as well as ac (transient component) which decays exponentially with time (const Y/R).

- Single line diagram — System components along with their data. (such as operating voltage, resistance & reactance etc)
- Impedance diagram → Components is represented by its equivalent ckt. (Tx line by nominal π m/f)
- Neutral earthing impedances do not appear in the diagram as balanced cond. are assumed.
- Reactance diagram — assumption $R \ll X$ so $S = 12Y$. errors in calculation will result in values higher than its actual and in some cases lead to purchase of protective gear with a higher rating than required.

①.

Symmetrical components

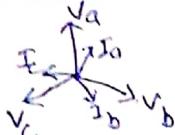- Balanced system \rightarrow  three phases (N & T), each have equal magnitude and displaced by 120° by each other.
- Knowledge of $V \& I$ in one phase is sufficient to completely determine voltages and currents in the other two phases.
- Real and Reactive powers are simply three times the corresponding per phase values.
- Unbalanced system is the result of balanced system due to ~~to~~ to unsymmetrical fault.
- Symmetrical component Analysis :- The impedances presented by various power system elements (Syn gen, T/F, TA line etc) to symmetrical components are decoupled. from each other resulting in independent system mws for each components (balanced set).

- 3 ϕ (3L) fault - 5%.

$$L-L-U = 10\%$$

$$LL = 15\%$$


$$L-U = 70\%$$

- 3- ϕ symmetrical fault analysis is carried out by Symmetric component theory. which has only mathematical meaning. not electrical meaning bcz only in +ve Seq. component we take source but for zero and -ve seq component no voltage source. so this is passive mws. but we show that a -ve & zero seq current flowing.

Symmetrical Components.


$$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} I_{a0} \\ I_{b0} \\ I_{c0} \end{bmatrix} + \begin{bmatrix} I_{a1} \\ I_{b1} \\ I_{c1} \end{bmatrix} + \begin{bmatrix} I_{a2} \\ I_{b2} \\ I_{c2} \end{bmatrix}$$

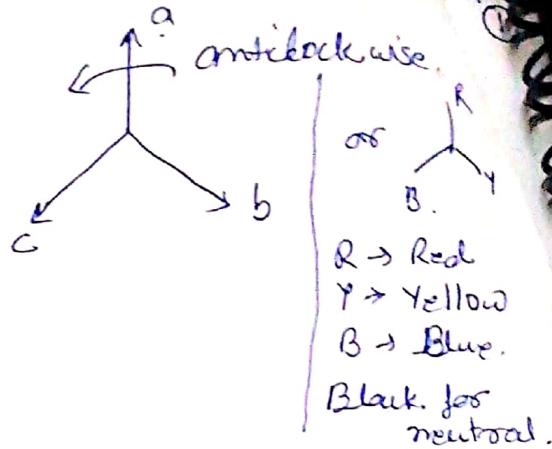↓
 Unbalanced condn
 zero seq
 +ve seq
 -ve seq.
 3. sets of balanced condn:-
 a
 b
 c




Positive Sequence Components.

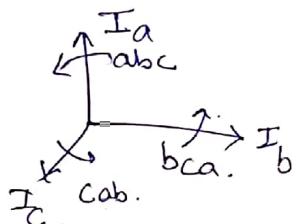These balanced components vectors have same sequence as original unbalanced vectors.



anticlockwise dirⁿ.

Unbalanced. original
vector.

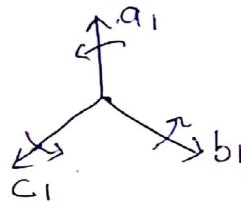

anticlockwise dirⁿ.
Same as actual.
Unbalanced. vector.

'a' operator.

$$a = 1 \angle 120^\circ = -0.5 + j0.866$$

$$a^2 = 1 \angle 240^\circ = -0.5 - j0.866$$

$$a^3 = 1 \angle 360^\circ = 1$$

$$1 + a + a^2 = 0$$


$$a^* = a^2 \quad | 1 + a^2 =$$

$$(a^2)^* = a$$

$$1 - a^2 = \sqrt{3} \angle 30^\circ$$

Matrix form
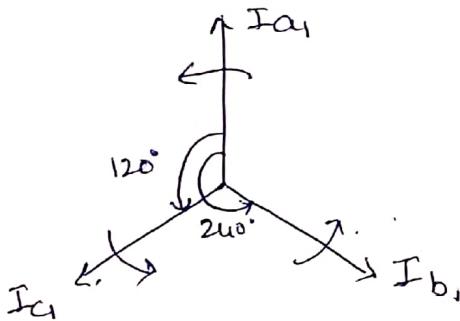
$$= \begin{bmatrix} 1 \\ a^2 \\ a \end{bmatrix} I_{a1}$$



$$I_{a1} = I_{a1} \angle 0^\circ$$

$$I_{b1} = I_{a1} \angle 240^\circ = a^2 I_{a1}$$


$$I_{c1} = I_{a1} \angle 120^\circ = a I_{a1}$$

$\therefore I_{b1} = I_{a1} \angle 240^\circ \rightarrow I_{b1}$ lead 240° b/f I_{a1}
 I_{a1} more 240° in dirⁿ of original by
 120° to reach I_{b1} .

↳ We can avoid if b and c phase component and operating only on a phase by operators 'a'.

↳ The operator 'a' transforms the b and c phase components into a phase components such that we can work on single phase basis.

Negative seq. components.

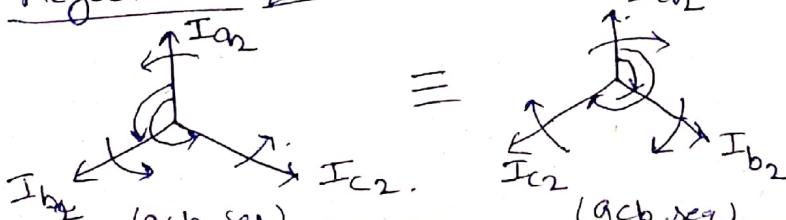

$$I_{a2} = I_{a2} \angle 0^\circ$$

$$I_{b2} = I_{a2} \angle 120^\circ = a I_{a2}$$

$$I_{c2} = I_{a2} \angle 240^\circ = a^2 I_{a2}$$

$$= \begin{bmatrix} 1 \\ a \\ a^2 \end{bmatrix} I_{a2}$$

①

②

zero seq. components:-

$$\begin{array}{c} \uparrow \quad \uparrow \quad \uparrow \\ I_{a_0} \quad I_{b_0} \quad I_{c_0} \end{array} \quad I_{R0} = I_{Y0} = I_{B0} = \begin{bmatrix} 1 \\ 1 \\ 1 \end{bmatrix} I_{R0}$$

No phase diff. ∵ operator 'a' is not required. bcz no phase difference.

→. +ve seq.

$$\begin{aligned} I_a &= I_{a_0} + I_{a_1} + I_{a_2} = \xrightarrow{I_{a_0}} \\ I_b &= I_{b_0} + I_{b_1}^{\xrightarrow{a^2 I_{a_0}}} + I_{b_2}^{\xrightarrow{a I_{a_1}}} \Rightarrow \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} I_{a_0} \\ I_{a_1} \\ I_{a_2} \end{bmatrix} \\ I_c &= I_{c_0} + I_{c_1}^{\xrightarrow{a I_{a_0}}} + I_{c_2}^{\xrightarrow{a^2 I_{a_1}}} \end{aligned}$$


$$[A]^{-1} = \frac{\text{Adj}[A]}{|A|} \Rightarrow [I]_{abc} = [A] [I]_{012}$$

$$\text{Adj}[A] = \text{co-factor matrix.} \Rightarrow [I]_{012} = [A]^{-1} [I]_{abc}$$

$$\begin{bmatrix} + & - & + \\ - & + & - \\ + & - & + \end{bmatrix} \Rightarrow \begin{bmatrix} I_{a_0} \\ I_{a_1} \\ I_{a_2} \end{bmatrix}_{012} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix}$$

Observation :-

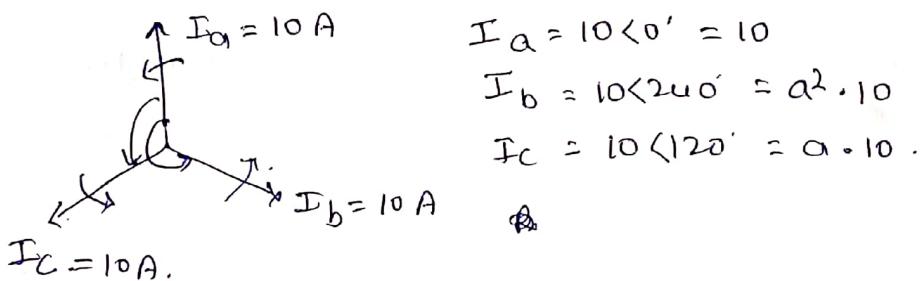①. In a balanced 3-φ system only +ve seq components are present.



$$I_a = 10 \angle 0^\circ = 10$$

$$I_b = 10 \angle 240^\circ = a^2 \cdot 10$$

$$I_c = 10 \angle 120^\circ = a \cdot 10$$

$$I_{a_1} = \frac{1}{3} [I_a + a I_b + a^2 I_c] = \frac{1}{3} [10 + a \cdot a^2 \cdot 10 + a^2 \cdot a \cdot 10] \\ = \frac{1}{3} [10(1 + a^3 + a^3)] = 10. \quad (\because a^3 = 1)$$

$$I_{a_2} = \frac{1}{3} [I_a + a^2 I_b + a I_c] = \frac{1}{3} [10 + a^2 \cdot a^2 \cdot 10 + a \cdot a \cdot 10] \\ = \frac{1}{3} [10 + 10 \cdot a + a^2 \cdot 10] \\ = \frac{1}{3} \times 10 [1 + a + a^2] = 0.$$

$$I_{a_0} = \frac{1}{3} [I_a + I_b + I_c] = \frac{1}{3} [10 + a^2 \cdot 10 + a \cdot 10] \\ = \frac{1}{3} \times 10 [1 + a + a^2] = 0.$$

- (2) In an unbalanced 3- ϕ system, all seq. components may be present.
- (3) +ve. and -ve. seq. current can't flow through neutral, only zero sequence current can appear in neutral wire.
- $$I_m = I_{m_0} + I_{m_1} + I_{m_2}$$
- $$I_{m_0} = (I_{a0} + I_{b0} + I_{c0}) = I_{a0} + I_{a0} + I_{a0} = 3 I_{a0}$$
- $$I_{m_1} = (I_{a1} + I_{b1} + I_{c1}) = I_{a1} + a^2 I_{a1} + a I_{a1} = I_{a1}(1+a+a^2)=0$$
- $$I_{m_2} = (I_{a2} + I_{b2} + I_{c2}) = I_{a2}(1+a+a^2)=0$$
- (4). For the flow of +ve. and -ve. seq. current the return path through ground is not compulsory, or the cond'n of neutral has got no effect for the flow of +ve/-ve seq. current.
- (5). For the flow of zero seq. current return path through ground is compulsory, or the cond'n of neutral (ungrounded, solidly grounded, reactance grounded) has got effect for the flow of zero seq. currents.
- (6). The original 3- ϕ system [a,b,c] is mutually joined n/w but the three seq. n/w's (+ve, -ve, & zero) are mutually disjoined. n/w's.

Observation:-

three phase system with neutral return

- (7) The sum of three line voltages will always be zero. Therefore, the zero sequence component of line voltages is always zero i.e.

$$V_{ab0} = \frac{1}{3}(V_{ab} + V_{bc0} + V_{ca}) = 0. \quad \left| \begin{array}{l} V_{ab} + V_{bc} + V_{ca} \\ = V_a - V_b + V_b - V_c + V_c - V_a = 0 \end{array} \right.$$

On the other hand, sum of phase voltages (line to neutral) may not be zero so that these zero seq comp Vars. may exist.

$$\therefore I_m = I_a + I_b + I_c \Rightarrow I_{0n} = \frac{1}{3}(I_a + I_b + I_c) = \frac{1}{3}I_m$$

Power Invariance

- (8). The sum of powers of the three symmetrical components equal the three phase power.

$$S = \sqrt{P} I_p^* \cdot [V]_{abc} [I]_{abc}^* \quad \left| \begin{array}{l} I^* \rightarrow \text{complex conjugate} \\ \text{bcz we need phase diff b/w} \\ \text{Voltage phase \& current phase.} \\ S = \text{complex power.} \end{array} \right.$$

$$= V_a I_a^* + V_b I_b^* + V_c I_c^*$$

$$\text{or. } [V]_{abc}^T [I]_{abc}^* = [A]^T [V]_{012}^T \quad \text{or. } [I]_{abc}^* = [[A] [V]_{012}]^*$$

$$\Rightarrow S = [A]^T [V]_{012}^T \cdot [A]^* [I]_{012}^*$$

$$\Rightarrow \text{whose rows are columns of original}$$

$$A^T = A^* \quad ; \quad A = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix}$$

$$A^T = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix}$$


A^* \rightarrow conjugate of a matrix is by taking conjugate of each element of A.

$$A^* = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \quad a^* = a^2 \quad (a^2)^* = a_1$$

$$\Rightarrow S = 3[V]_{012}^T U \cdot [I]_{012}^*$$


$$= 3[V_{a0} I_{a0}^* + V_{a1} I_{a1}^* + V_{a2} I_{a2}^*]$$

= Sum of Symmetrical comp power

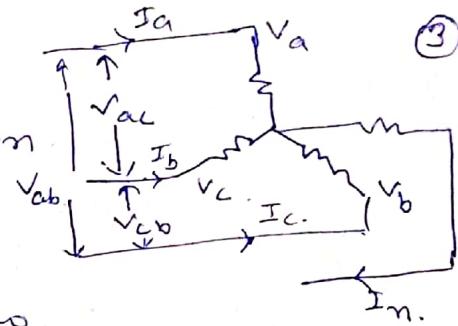

Q). A delta connected balanced resistive load is connected across unbalanced three phase supply as shown in fig. With current in lines A and B specified. find the symmetrical components of line currents. [Also find the symmetrical components of delta currents]. Do you mean currents in leg of Δ fault

Soln:-

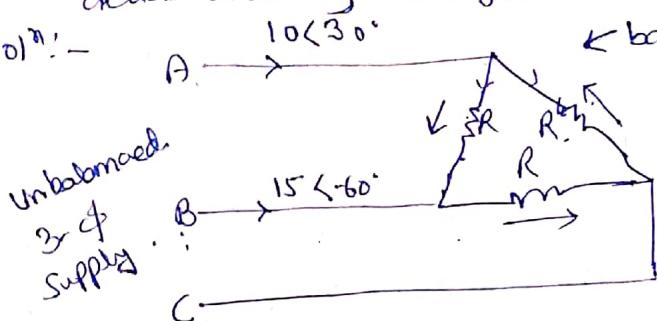

\leftarrow balanced resistive load.

\therefore load is balanced. — ①.

$$I_A + I_B + I_C = 0$$

$$\Rightarrow 10\angle 30^\circ + 15\angle -60^\circ + I_C = 0$$

$$\Rightarrow I_C = -16.2 + j8 = 18\angle 154^\circ A.$$

$$\begin{bmatrix} I_{A0} \\ I_{A1} \\ I_{A2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha & \alpha^2 \\ 1 & \alpha^2 & \alpha \end{bmatrix} \begin{bmatrix} I_A \\ I_B \\ I_C \end{bmatrix}$$

\downarrow unbalanced currents. — ②. $= \frac{1}{3} I_A$


$$I_{A0} = \frac{1}{3}(I_A + I_B + I_C) = \frac{1}{3} \times 0 = 0.$$

$$\Rightarrow I_{A1} = \frac{1}{3}[I_A + \alpha \cdot I_B + \alpha^2 I_C]$$

$$I_{A1} = \frac{1}{3}[10\angle 30^\circ + 15\angle -60^\circ + 120^\circ + 18\angle 154^\circ + 240^\circ] \\ = 10.35 + j3.3 = 14\angle 42^\circ A.$$


$$I_{A2} = \frac{1}{2}[I_A + \alpha^2 I_B + \alpha I_C] = \frac{1}{2}[10\angle 30^\circ + 15\angle -60^\circ + 240^\circ + 18\angle 154^\circ + 120^\circ] \\ = -1.7 - j4.3 = 4.65 \angle 248^\circ A.$$

Now.

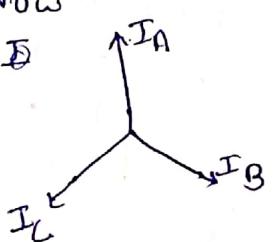

$$I_{A1} = I_A \angle 0^\circ \\ I_B = I_A \angle 240^\circ \\ I_C = I_A \angle 120^\circ$$
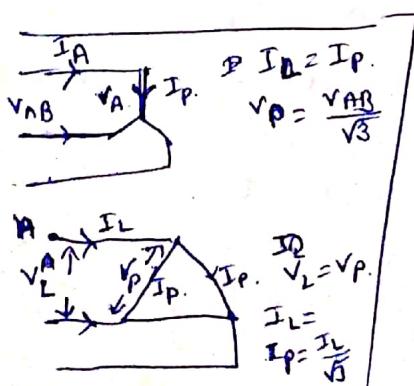
$$I_{A0} = 0. \quad I_{B0} = 0. \\ I_{A1} = 14\angle 42^\circ. \quad I_{B1} = 14\angle 42 + 240^\circ \\ I_{A2} = 4.65 \angle 248^\circ. \quad I_{B2} = 4.65 \angle 248 + 120^\circ \\ = 4.65 \angle 368^\circ \\ = 4.65 \angle 8^\circ.$$



$$I_{C0} = 0. \\ I_{C1} = I_A \angle 120^\circ = 14\angle 42^\circ + 120^\circ = 14\angle 162^\circ \\ I_{C2} = I_A \angle 240^\circ = 14\angle 42^\circ + 4.62(248^\circ + 240^\circ)$$

$$= 4.62 \angle 488^\circ = 4.62 \angle 128^\circ A.$$

$\frac{V_{AB}}{360} = 48.8^\circ$

Sequence impedances:

Generator $\rightarrow x_{00} < x_{02} < x_{01}$

T/F & Tx line $\rightarrow x_0 > x_1 = x_2$

Sequence Networks:- Gen (1) $\xrightarrow{3/1/0}$ Line (2) . 3- ϕ sym

(1) Generator representation: (1) |

\rightarrow N/w have 3- ϕ symmetry bcz of which current of particular seq passed. Voltage drop of some seq appear i.e. the elements posses only self impedance to seq currents. so seq whos are decoupled represented.

(1) Generator representation: (1) | Syn imp of gen = Z_1 of gen. $\left(Z_s \right)$

\rightarrow Sym m/c is designed, with symmetrical wedges. $= Z''$ (normally)

\rightarrow If armature resistance is assumed negligible, the positive seq impedance Z_1 is m/c equivalently offers a direct axis reactance whose values

$Z_1 = jX_d''$ (if 1 cycle transient as below considered). $\left[\begin{array}{l} \text{typical value} \\ Z_d \rightarrow Z_1 \\ Z_d \rightarrow 12 \text{ to } 14x \\ Z_0 \rightarrow 5 \text{ to } 7x \end{array} \right]$

$Z_{01} = jX_d'$ (if 3-4) $\left(\begin{array}{l} \text{typical value} \\ Z_d \rightarrow Z_1 \\ Z_d \rightarrow 12 \text{ to } 14x \\ Z_0 \rightarrow 5 \text{ to } 7x \end{array} \right)$

jX_d (if steady state condn)

\rightarrow If the m/c short ckt takes place from unloaded cond' the terminal voltage constitute the +ve seq voltage

\rightarrow If s.c.kt occurs from loaded cond', the voltage behind appropriate reactance (X'', X', X_s) constitute the +ve seq voltage.

\rightarrow The ref bus for the seq n/w is at ground potential bcz no current flows from ground to neutral.

\rightarrow -ve seq field rotates in the opposite dirⁿ to that of the +ve seq field. and, therefore, at double

the stator frequency one. therefore induced in the -ve seq mmf

\rightarrow The is alternately presented with reluctance of direct and quadrature axes. The -ve seq imp (considering damper wedge & field) $Z_2 = j \frac{x_1'' + x_2''}{2} X_d$, $|Z_2| < |Z_1|$


→ The flow of zero seq currents creates three moments which are in time phase but are distributed in space by 120° . The resultant air gap field caused by zero seq currents is therefore zero. Hence only motor wdg leakage reactance caused by flow of Z_{0g} zero seq currents.

$$Z_{0g} \text{ zero seq currents. } [Z_{0g} < Z_2 < Z_1]$$


X_{motor} is slightly less than X_m

$$V_{ao} = -3Z_n I_{ao} - Z_{0g} I_{ao} = -(3Z_n + Z_{0g}) I_{ao}$$


$$\Rightarrow Z_0 = 3Z_n + Z_{0g}$$

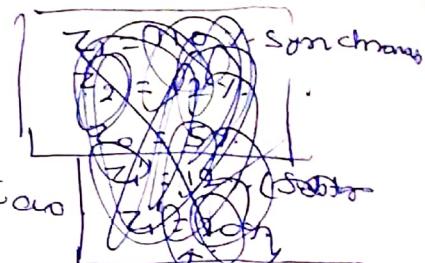

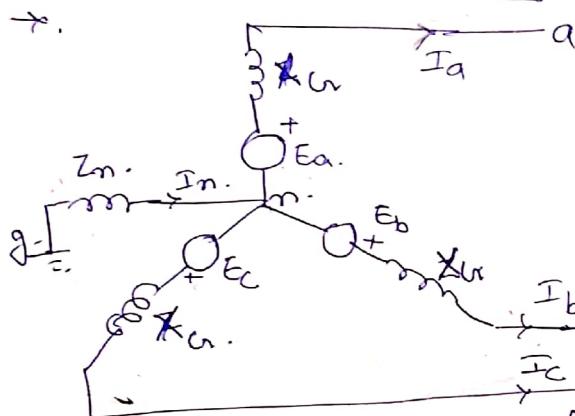values for 5 MVA
6.6 kV, 3000 rpm
rated gen.




3-phase gen with grounded neutral.

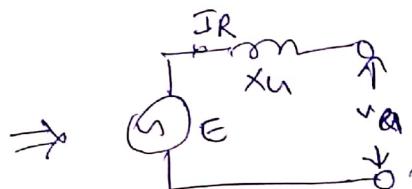


original m/w.
without grounded
neutral.
(anticlockwise).


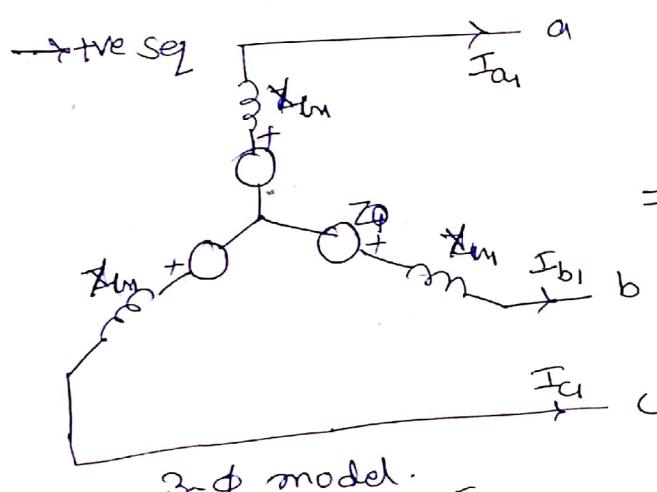
gen rotates in anticlockwise
dir so generates voltage.
so voltage is represented



3-phase model.

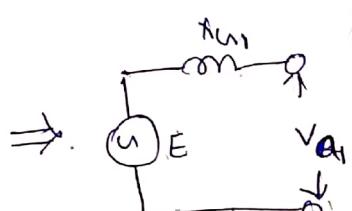


+ve Seq m/w.
anticlockwise.

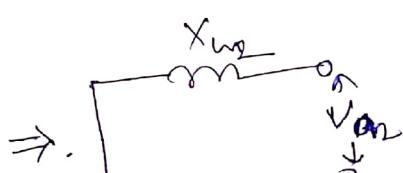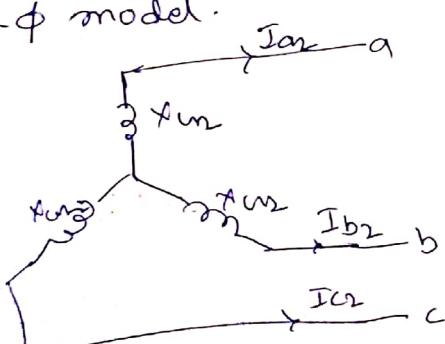


$$V_{a2} = I_{R2} X_{m2}$$

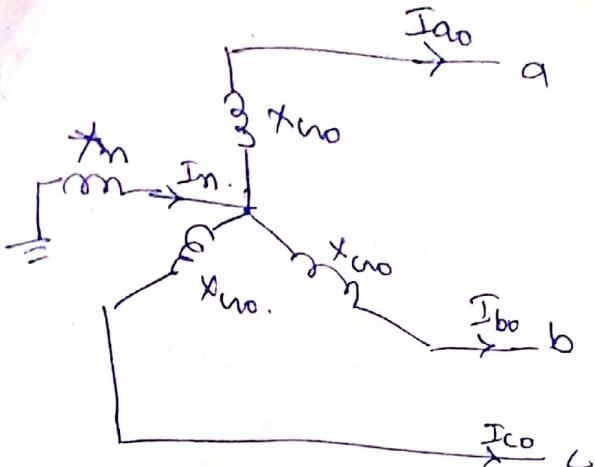motor must rotate in clockwise
dir. but actually rotates in
anticlockwise dir. So this
is not possible. at some
time. so voltage is zero.



\Rightarrow

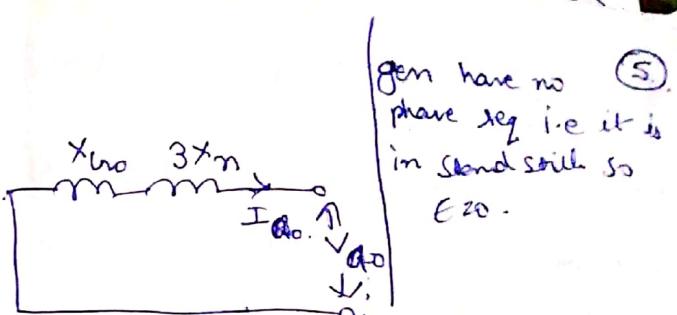


gen have no phase seq i.e. it is in standstill so E_{20} . (5)


$$V_{ao} = -(3X_n + X_{ba}) I_{ao}$$

$$X_0 = 3X_n + X_{ba}$$


- The motor rotates in anticlockwise dirⁿ and produced voltage in RYB phase. for +ve seq voltage we must rotate motor in anticlockwise dirⁿ i.e. in RYB.
- For -ve sequence voltage motor must rotate in clockwise dirⁿ but motor already rotates in anticlockwise dirⁿ so this is not possible at same time so -ve seq voltage is zero.
- For zero seq voltage generator must have no phase seq i.e. it is in standstill so in this case E_{20} .
- The generator wdg is always in Y bcz in Δ connection circulating currents flows which heats the gen wdg so problem of insulation.
- In zero seq n/w \rightarrow if neutral is ungrounded then it is represented by open ckt.
- Solidly grounded. \rightarrow short ckt
- grounded by some reactance (X_n) \rightarrow $3X_n$ in series with X_{ba}

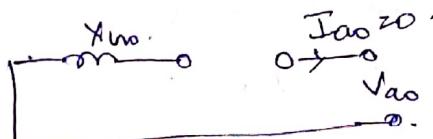

ungrounded.

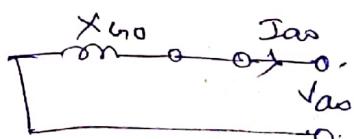

Solidly grounded.

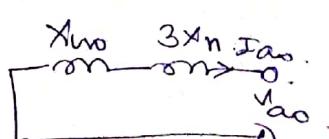

grounded by X_n .


② Transformer Representation

318

①

→ Phase shift in Star-delta T/F.

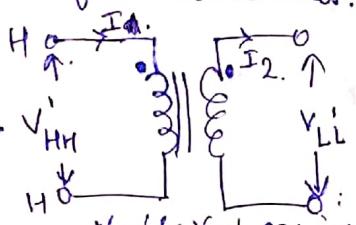
→ +ve & -ve seq voltages and currents undergo a phase shift in passing through a star- Δ transformer which depends on the labelling of terminals.



→ Polarity of $V_{HH}' = V_{LL}'$.



→ magnetizing current neglected.

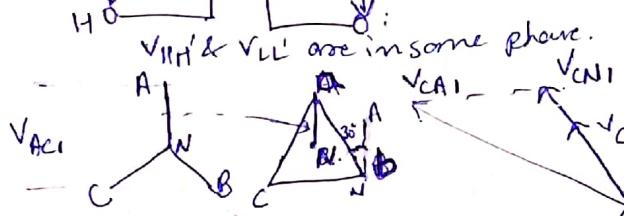→ T/F excited with V_{AB1} so I_{AB1} flows.



$$V_{AN1} = \frac{V_{AC1}}{\sqrt{3}} = \frac{V_{AB1}}{\sqrt{3}}$$

V_{AC1}

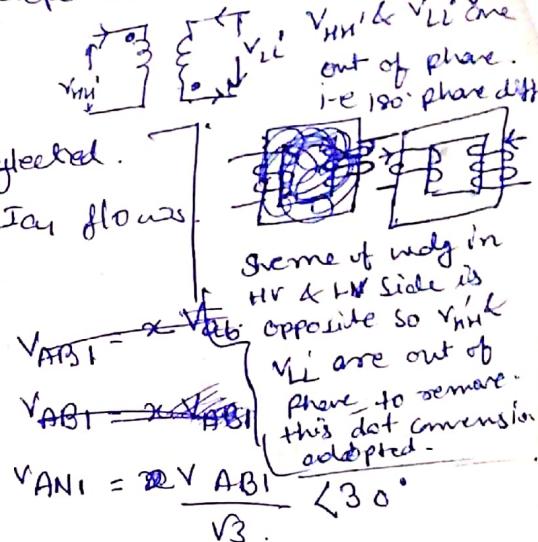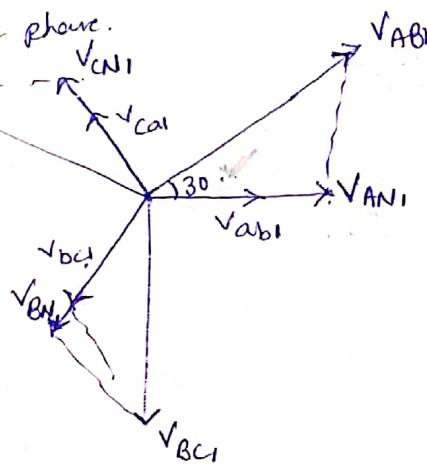

$$V_{AN1} = \frac{V_{AB1}}{\sqrt{3}} \angle 30^\circ$$

$$(Y) V_{AB} = (Z) \propto V_{AB} \angle 30^\circ,$$

\propto = phase transformation ratio.

→ The positive sequence line voltages on star side lead the corresponding voltages on the delta side by 30° (The same result for phase voltages). and same result for current also.



→ When T/F excited by -ve seq voltages. (Y - Δ T/F.

Y → HV side.

Δ → low voltage side.

The positive seq quantities on the HV side lead their corresponding positive seq quantities on the LV side by 30° . The reverse is true of -ve seq quantities wherein HV quantities lag the correspondingly LV quantities by 30° .

i.e.,

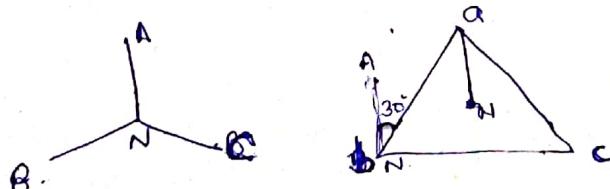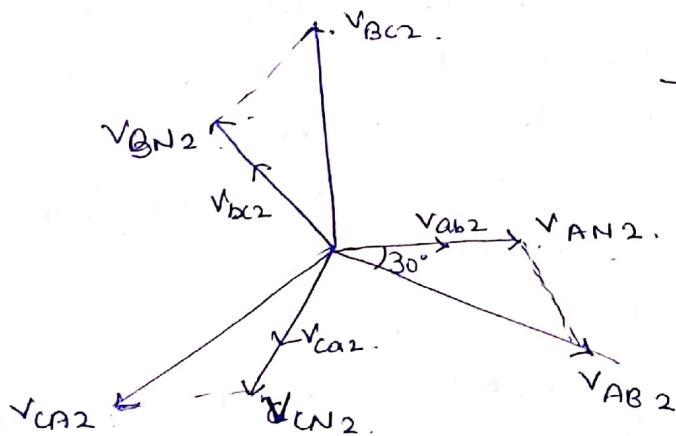

star lead 30° by Δ

32

Sequence impedances and. Nethooke of transformer.


$$\boxed{Z_0 \Rightarrow Z_1 = Z_2 = Z_{\text{leakage}}}$$

$Z_0 \rightarrow$ rated phase impedance.
usually the value corresponding to I_N
measurement is carried out with $3 \times I_N \rightarrow$ always not true.

Since T/F is a static device, the leakage impedance does not change with alternation of phase seq of balanced applied voltages.

- Z_0 slightly differ from Z_1 & Z_2 .
- zero seq magnetizing current is higher in core than shell type.

zero seq N/W of T/F
Imp observation

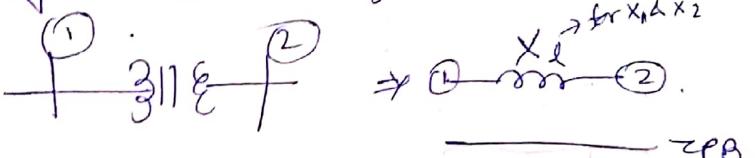

$$I_{NL} = 4-5\% I_{fl.}$$

+ve / -ve zero seq N/W


- All seq mags of T/F is represented by series reactance.
- The type of wedg and cond' of neutral have got no effect on representing the T/F seq mags. (+ve & -ve).
- The type of wedg and cond' of neutral have got effect in representing zero seq n/w.

zero Seq N/Ws of T/Fs.


three imp observation.

① When magnetizing current is neglected, Transformer primary would carry current only if there is current flow on the secondary side.

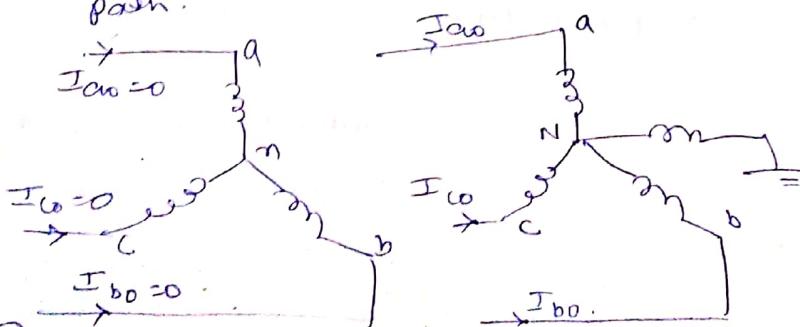
② Zero seq currents can flow in star leg of star only if star pt is grounded i.e. which provide return path.



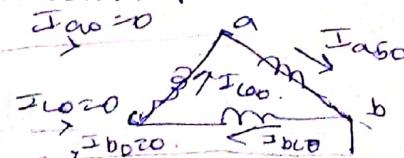③ In A connection No return path so in the leg of A of no zero seq current.



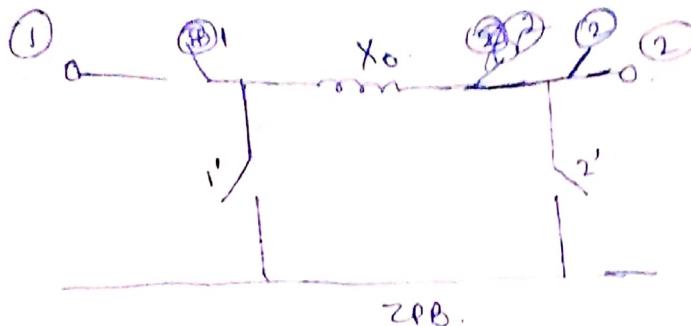Switch Diagram: Used to represent T/F in zero seq mho. ①








- 1' → Primary switches.
- 2' → Secondary switches.
- 12 → Series switch
- 1'2' → Shunt switch.


ZPB. → When the T/F is star connected.

→ A Series switch is closed when the T/F is star connected with neutral grounded.

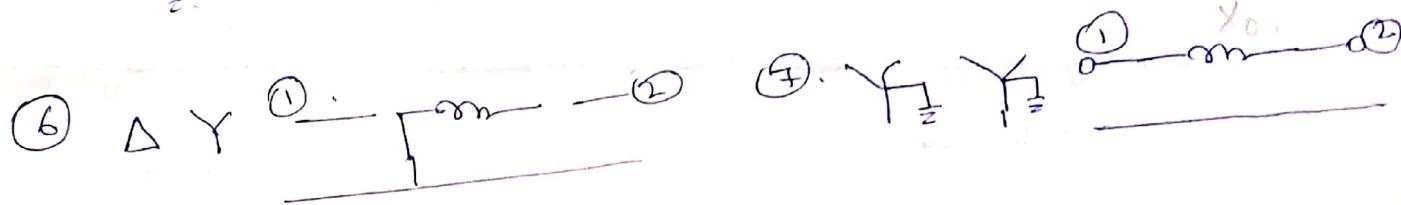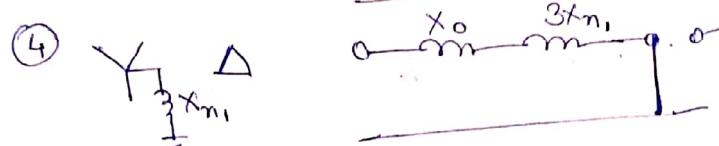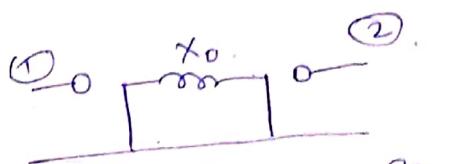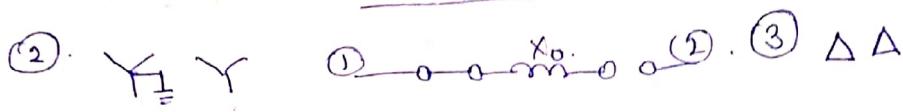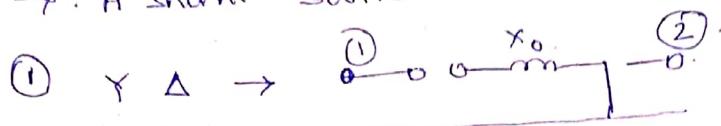→ A shunt switch is closed when the T/F is Δ connected.




Transmission line Representation.

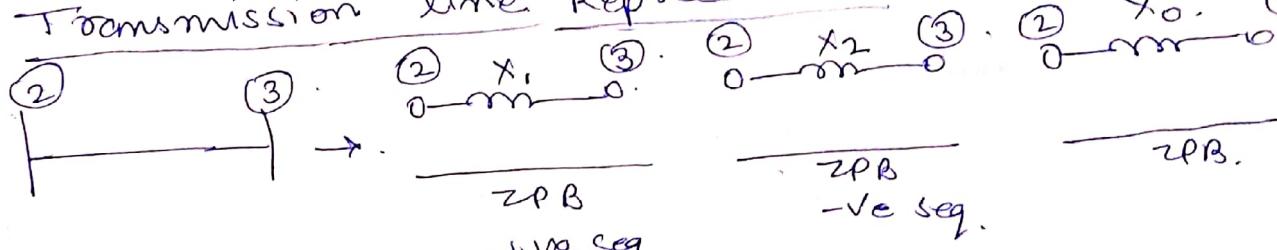

Sequence impedances And Networks of synchronous

~~Transmission lines.~~

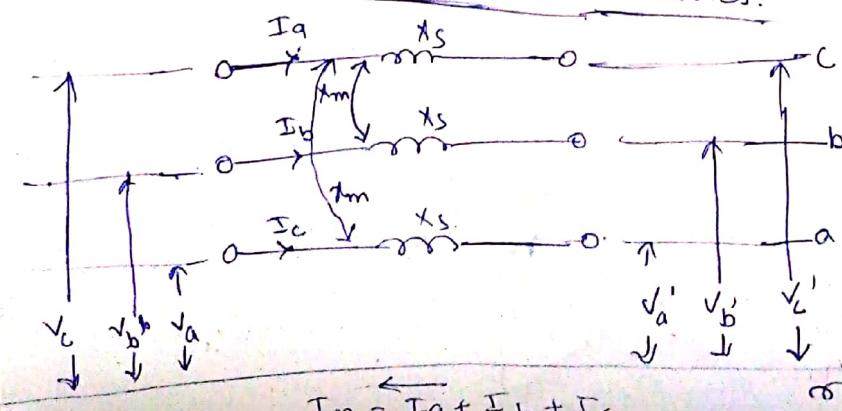

Fully transposed lines.

Carrying unbalanced currents.

return path is sufficiently away to ignore the mutual effect

return path (ZPB).

$$V_a - V_a' = j I_a x_s + j I_b x_m + j I_c x_m$$

$$V_b - V_b' = j I_b x_s + j I_a x_m + j I_c x_m$$

$$V_c - V_c' = j I_c x_s + j I_a x_m + j I_b x_m$$

$$\Rightarrow \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} - \begin{bmatrix} V_a' \\ V_b' \\ V_c' \end{bmatrix} = j \begin{bmatrix} x_s & x_m & x_m \\ x_m & x_s & x_m \\ x_m & x_m & x_s \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix}$$

$$\Rightarrow [V_p] - [V_p'] = Z [I_p]$$

$$\Rightarrow A (V_s - V_s') = Z A I_s$$

$$\Rightarrow (V_s - V_s') = A^{-1} Z A I_s.$$

Symmetrical component

$$\Rightarrow A^{-1} Z A = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} j x_s & j x_m & j x_m \\ j x_m & j x_s & j x_m \\ j x_m & j x_m & j x_s \end{bmatrix} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix}$$

$$= j \begin{bmatrix} x_s + 2x_m & 0 & 0 \\ 0 & x_s - x_m & 0 \\ 0 & 0 & x_s - x_m \end{bmatrix}$$

$$\Rightarrow (V_s - V_s') = A^{-1} Z A I_s.$$

$$\Rightarrow \begin{bmatrix} V_0 \\ V_1 \\ V_2 \end{bmatrix} - \begin{bmatrix} V_0' \\ V_1' \\ V_2' \end{bmatrix} = j \begin{bmatrix} x_s + 2x_m & 0 & 0 \\ 0 & x_s - x_m & 0 \\ 0 & 0 & x_s - x_m \end{bmatrix} \begin{bmatrix} I_0 \\ I_1 \\ I_2 \end{bmatrix}$$

$$= \begin{bmatrix} Z_0 & 0 & 0 \\ 0 & Z_1 & 0 \\ 0 & 0 & Z_2 \end{bmatrix} \begin{bmatrix} I_0 \\ I_1 \\ I_2 \end{bmatrix}$$

$$\Rightarrow Z_0 = x_s + 2x_m.$$

$$Z_1 = x_s - x_m = Z_2$$

$$\Rightarrow Z_0 > Z_1 = Z_2$$

$$[V]_{RyB} = [X]_{RyB} [I]_{RyB}$$

$$[A][V]_{012} = [X]_{RyB} [A] [I]_{012}$$

$$[V]_{012} = \underbrace{[A]^{-1} [X]_{RyB}}_{[X]_{012}} [A] [I]_{012}$$

$$[X]_{012}$$

$$[V]_{012} = [X]_{012} [I]_{012}$$

$$[X]_{012} = [A] [X]_{RyB} [A]$$

$$= \begin{bmatrix} x_s + 2x_m & 0 & 0 \\ 0 & x_s - x_m & 0 \\ 0 & 0 & x_s - x_m \end{bmatrix}$$

off diagonal element of seq matrix is zero i.e. seq n/w is disjoint w/u.

$$st$$

$$I_0, V_0, Z_0 \rightarrow \text{zero seq.}$$

$$I_1, V_1, Z_1 \rightarrow \text{one seq.}$$

$$I_2, V_2, Z_2 \rightarrow \text{two seq.}$$

$$+ve, -ve, \& \text{zero seq. m/w of T/F, Tx. etc}$$

$$\& \text{syn. m/w. all are decoupled m/w.}$$

(P) watt
→ Active Power or Real P , actual P , true power, wattfull P ; useful P)

↳ which is really transferred to load; $1W = 1V \times 1A$.

$$P(\text{DC ckt}) = VI$$

$$P(\text{AC ckt}) = VI \cos\theta \quad (\rightarrow \phi \text{ AC ckt})$$

$$\begin{aligned} P(3\phi) &= \sqrt{3} V_L I_L \cos\theta \quad (3\phi \cdot \text{AC ckt}) \\ &= 3V_{ph} I_{ph} \cos\theta. \end{aligned}$$

$$P = \sqrt{S^2 - Q^2} = \sqrt{VA^2 - VAR^2}$$

S → apparent P .

Q → reactive P .

Reactive Power Q .

watless power, wattless power.

↳ Power that continuously bounces back and forth b/w source and load.

↳ may be absorbed or returned in load

↳ energy first stored & then released in the form of mag field or electrostatic field in case of inductor and capacitor resp.

$Q = VI \sin\theta$; +ve for inductive load.
L Voltampere -ve for Capacitive load.

$$1VAR = 1V \times 1A$$

→ Reactive P $\theta \rightarrow$ phase angle.

$$Q = VI \sin\theta$$

$$VAR = \sqrt{VA^2 - P^2} = \sqrt{S^2 - P^2} = \sqrt{VA^2 - W^2}$$

→ Apparent Power (S)

$$S = VI \quad (\theta \rightarrow \text{ignored})$$

↳ rms value.

$$1VA = 1V \times 1A$$

Pure resistive ckt $\rightarrow S = P$.

reactive ckt $\rightarrow S \propto P$

$$|S| = \sqrt{P^2 + Q^2} \neq P$$

length of complex power is apparent P .

Complex Power (S).

$$S = P + jQ$$

↳ KVVAR.

↳ Volt ampere reactive.

$$S = VI^*$$

I^* = Conjugate of Complex current

$$S = VI^* = V \cos\theta + jV \sin\theta$$

Complex Power in Capacitive loads.

$$Z = R - jX_C$$

Capacitive load.
provide leading load.
Wants $j\omega C$ to cancel R & jX_C .

$$I = I_p + jI_Q$$

$$\cos\theta = R/|Z| \text{ (leading).}$$

$$I^* = I_p - jI_Q$$

$$S = P - jQ$$

Complex Power in inductive loads.

$$Z = R + jX_L$$

$$I = I_p - jI_Q$$

$$\cos\theta = R/|Z| \text{ (lagging).}$$

$$I^* = I_p + jI_Q$$

$$S = P + jQ$$

inductive load,
provide lagging
voltage i.e. added reactance
the overall power factor.

~~I_{mm} max^m momentary short ckt current, correspond to transient comp negl.~~


~~$\sin(A - B) = \sin A \cos B - \sin B \cos A$, Gaussing.~~

$$I_{mm} = \frac{\sqrt{2} V}{Z} \sin(\omega t + \alpha - \theta)$$

$$= \frac{\sqrt{2} V}{Z} \sin(\omega t - (\theta - \alpha))$$

$$= \frac{\sqrt{2} V}{Z} \sin \omega t \cos(\theta - \alpha)$$

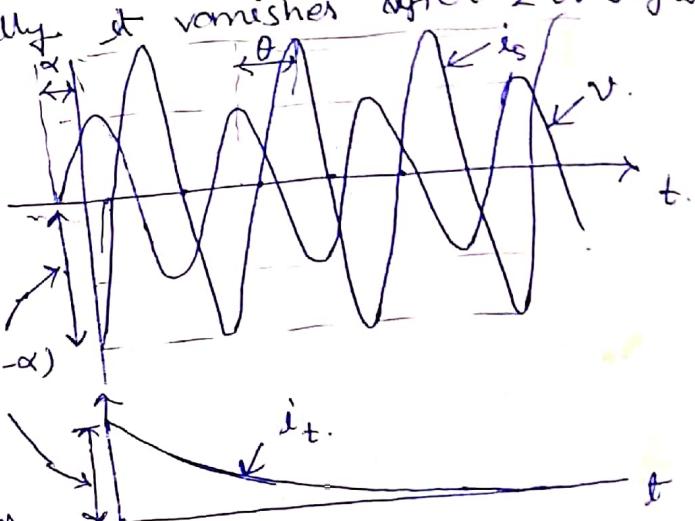The 2nd term is a transient which vanishes theoretically after infinite time. But practically it vanishes after 2 or 3 cycles.



$I_{mm} = \text{max}^m$ momentary current.


If decay of i_t in short time is negligible, then:

$$\text{at } \omega t \approx 0: I_{mm} = \frac{\sqrt{2} V}{|Z|} \sin(\theta - \alpha) + \frac{\sqrt{2} V}{|Z|} \rightarrow \text{transient.}$$

~~(transient state)~~
∴ Tx line R is small so $\theta \approx 90^\circ$.

$$I_{mm} = \frac{\sqrt{2} V}{|Z|} \cos \alpha + \frac{\sqrt{2} V}{|Z|}$$

$$(I_{mm})_{\text{max}^m \text{ possible}} = \frac{\sqrt{2} V}{|Z|} + \frac{\sqrt{2} V}{|Z|} = 2 \cdot \frac{\sqrt{2} V}{|Z|}$$

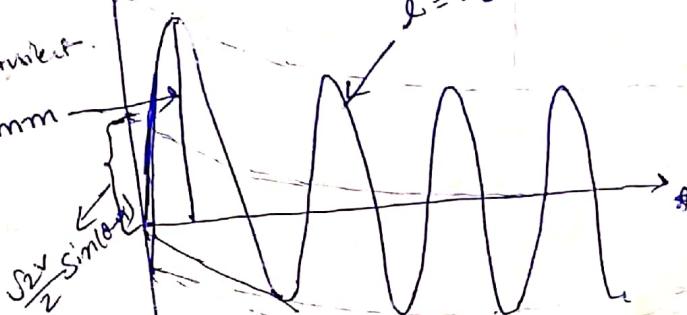

wave waveform of SC current in Tx line.

= ~~2~~ twice the max^m symmetrical short ckt current (doubling effect).


→ Initial de component decay over time, eventually reaching zero.
DC comp + symmetrical. SC current = Asymmetrical short ckt current

Short circuit of a synchronous machine (on No load).


Under steady state short ckt condⁿ, the armature reaction of synchronous generator produced demagnetizing flux.

$X_d \rightarrow$ direct axis syn reactance (salient pole m/c).

$R_a \rightarrow$ Small (neglected).


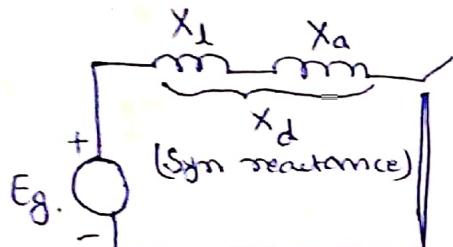


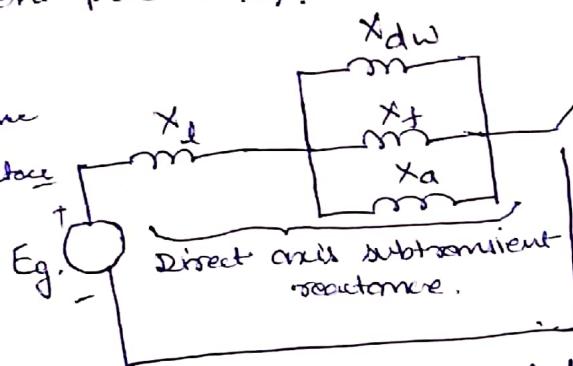$X_l \rightarrow$ leakage reactance
 $X_a \rightarrow$ armature reactance



(a) Steady state short ckt model of a syn m/c.

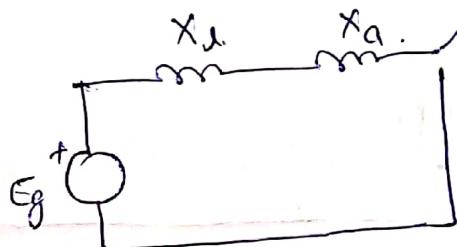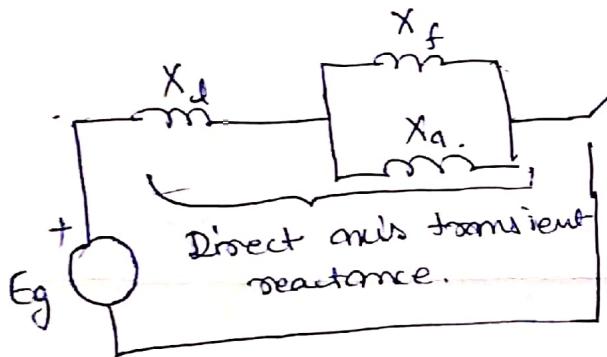(b) approximate ckt model during subtransient period. of short ckt.



(c) Approximate ckt model during transient period.

Finally same as steady state model.

→ Sudden short ckt (3-φ) of sym gen initially operated under open circuit condition (no load condⁿ).

→ The DC-off-set currents appear in all the three phases each with a different magnitude since the point on the voltage wave at which short ckt occurs is different for each phase. These DC off-set currents are accounted for separately on an empirical basis.

Based on observation so. for short ckt studies concentrate only on symmetrical (sinusoidal) short ckt currents only.

→ Sinusoidal steady state current.

→ On the event of a short ckt the ~~Is~~ I_s is limited by X_l . Since the air gap flux can't change instantaneously (theorem of constant flux linkages), to counter the demagnetization of the armature short ckt currents, currents appear in the field wdg as well as damper

damper wedge during initial period of short circuit in a diode to help the main flux. These current decay in accordance with the wedge constants.

Time const of Damper wedge (x_d'') \ll field wedge (x_f).

→ The reactance in initial period of short circuit x_d''


$$x_d'' = x_d + \frac{1}{\frac{1}{x_a} + \frac{1}{x_f} + \frac{1}{x_{dw}}} \quad (\text{Subtransient reactance})$$

$$x_d' = x_d + (x_a || x_f) = x_d + \frac{1}{\frac{1}{x_a} + \frac{1}{x_f}} \quad (\text{transient reactance})$$

x_d → synchronous reactance (Steady condn).

$$x_d'' < x_d' < x_d$$

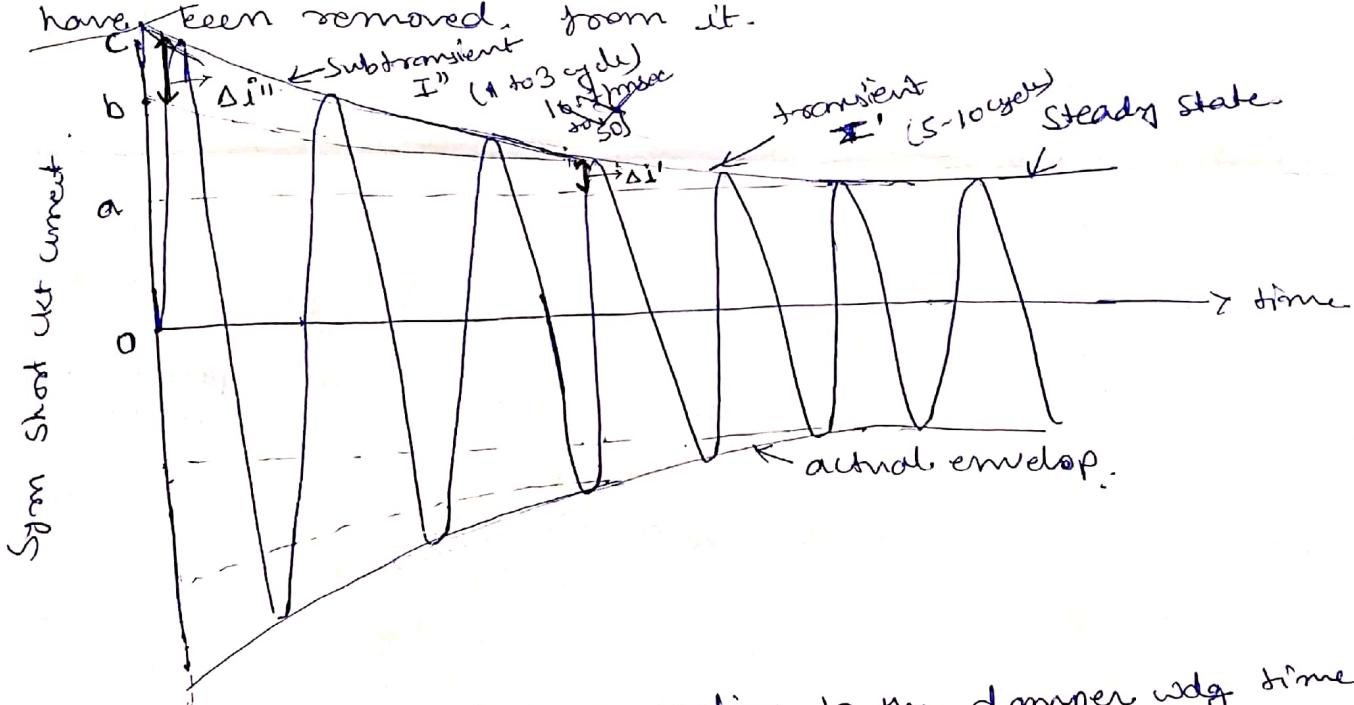→ Short circuit current of syn m/c after the DC-off set current have been removed from it.



→ $\Delta i'' (x_{dw})$ decays fast according to the damper wedge time const.

→ $\Delta i'$ decays in accordance with field time const.

$$\rightarrow |I| = \frac{0a}{\sqrt{2}} = \frac{|E_g|}{x_d} ; |I'| = \frac{0b}{\sqrt{2}} = \frac{|E_g|}{d x_d' B} ; |I''| = \frac{0c}{\sqrt{2}} = \frac{|E_g|}{x_d''}$$

$|I|$ → Steady state current (rms).

$|I'|$ = Transient current (rms) excluding DC component.

$|I''|$ = Subtransient current (rms) excluding DC component.

x_d = direct axis synchronous reactance.

x_d' = direct axis transient reactance.

x_d'' = direct axis subtransient reactance.

$|E_g|$ = per phase no load voltage (rms).

$\alpha_a, \alpha_b, \alpha_c$:

Both $\Delta i''$ & $\Delta i'$ decay exponentially. as

$$\Delta i'' = \Delta i''_0 \exp(-t/T_{dw}) = \Delta i''_0 e^{-t/T_{dw}}$$

$$\Delta i' = \Delta i'_0 e^{-t/T_f}$$

$$T_{dw} \ll T_f$$


→ Normally both generator and motor subtransient reactances are used to determine the momentary current flowing on occurrence of short ckt.

→ To decide interrupting capacity of CB. except those which open instantaneously.

Subtransient reactance is used for generator.

Transient reactance is used for motor. Numerical ① & ②.

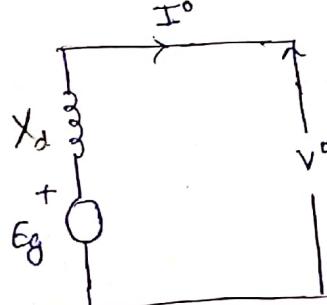Short ckt of a loaded synchronous machine.



Ckt model of loaded m/c.


(Steady state condn).

E_g → induced emf,

V^o → terminal voltage.


$I^o, V^o \rightarrow$ prefault voltage
Prefault current

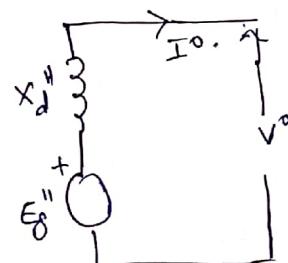→ When short ckt occurs at the terminals of this m/c.



① Ckt model for computing subtransient current.

$$E_g'' = V^o + j I^o X_d''$$

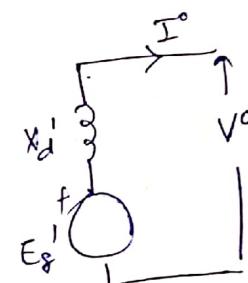

② Ckt model for computing transient current.

$$E_g' = V^o + j I^o X_d'$$

If I^o is zero (no load case), $E_g'' = E_g' = E_g$. the no load voltage ckt model as in previous case (no load case)

For motor : Eg replaced by Em. and. sign of I^o reversed.


$$E_m'' = V^o - jI^o X_d''$$

$$E_m' = V^o - jI^o X_d'$$

- Whenever we are dealing with short ckt. of arm interconnected system . the synchronous machines (gen and motors) are replaced by their corresponding ckt models.

Q. 1 For the radial network shown in fig :

Ckt

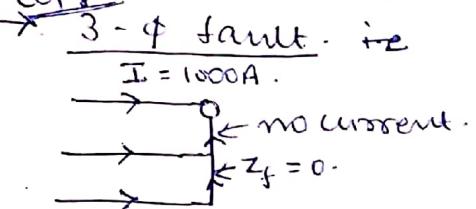

$Z_f = 0$ bcz no current flowing through this

In this fault, a high balanced current is flowing through phases but not through connecting object of 3- ϕ line bcz it is in balanced. condn.

Here $Z_f = 0$ so called. dead. short ckt. The impedance upto fault location limit the fault current not Z_f .


→ If Z_f has finite value then called. as a short ckt.

→ Z_{PB} → The neutral of a balanced system.

↳ zero power bus

The linear diagram P.S into per unit equivalent reactance diagram.

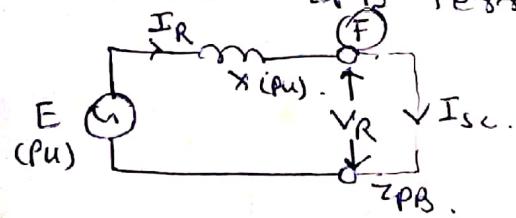- ① Convert the given linear diagram P.S into per unit equivalent reactance diagram.
- ② Look for the faulted. bus terminal. F & Z_{PB} . (zero Power Bus).
- ③ Reduced the P.S into thvenin's equivalent ckt. across F and. Z_{PB} terminal.



on single phase basis,
for R-phase

V_R = Voltage across the faulted. bus. terminal

E = Thevenin's equivalent prefault voltage.

X = Thevenin's equivalent reactance.

$$I_{sc} = I_R = I_{f, 3\phi} = \frac{E}{X} = I_y = I_B$$





$V_R = V_y = V_B = 0$. (Voltage across short ckt = 0)

→ Bcz of majority of time generators represented by 1pu voltage so thevenin's equivalent is 1pu. so. $E_g = 1\text{pu} = E_{th}$

$$I_{f, 3\phi} = \frac{E}{X} = \frac{1}{X} \text{ pu.} ; P_{f, 3\phi} = E \cdot I_{sc} = 1 \cdot \frac{1}{X} ; \text{ or } P_{f, 3\phi} (\text{pu}) = \frac{P_{f, 3\phi}}{P_{B, \text{pu}}}.$$

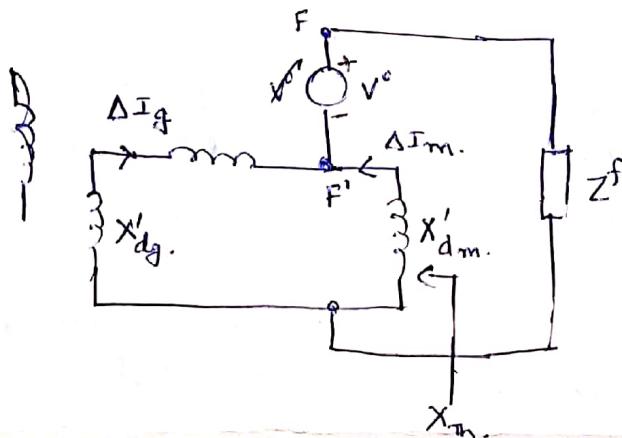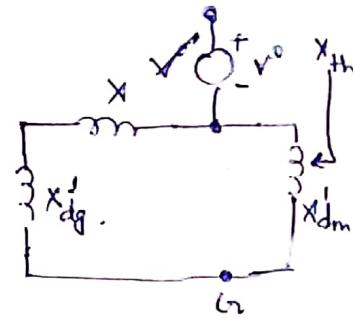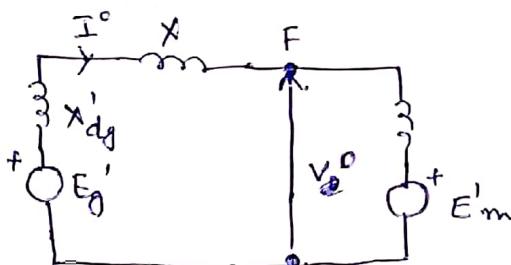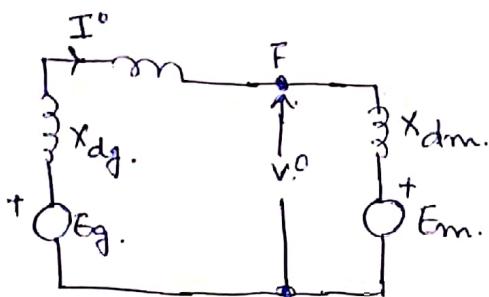(4)

In m/c one represented by their transient reactances (or subtransient reactances if subtransient currents are of interest) in series with voltages behind transient reactances. This change does not disturb the prefault current I^0 and, prefault voltage V^0 (at F).



X_{Th} → thevenin equivalent.

V^0 → Prefault voltage.

I^0 → Prefault current

I_f → fault current

X'_{dg} → gen transient reactance.

X'_{dm} → motor transient reactance.

I^0 does not appear in the passive thevenin imp n/w.

→

$$\Delta I_m = \frac{X'_{dg} + X}{X'_{dm} + X + X'_{dg}} I^0$$

$$I_g^f = I^0 + \Delta I_g$$

Post fault

$$I_m^f = -I^0 + \Delta I_m$$

Post fault.

In case of load
load in MW kVA
 $I_0 = \frac{MW}{V^0 \times P.f.}$

$$\text{Post fault voltage } V^f = V^0 + (-jX_{Th} I_f) = V^0 + \Delta V$$

→ Assumption (1). All prefault voltage magnitudes are 1 pu.


(2) All prefault currents are zero. (no load condn).

→ changes in current caused by short ckt are quite large, of the order of 10-20 pu and are purely reactive; whereas the prefault load currents are almost purely real.

+ Hence the total postfault current can be largest comp magnitude (caused by fault). This satisfy assumption (2).

- Due to severest demagnetization effect during fault V is zero.
So we need prefault voltage or thevenin's voltage.
 - Short ckt kVA or fault level = $V_{rated} \times I_{sc}$.
 - The main appln of conducting short ckt and fault analysis is to design the breaking capacity of CB.
 - A short ckt is a high current, low voltage, highly lagging, low p.f. phenomenon.
 - Since P.S is not starting for operation before protecting devices are installed and CB breaking capacity is found by short ckt study so short ckt study is performed. first now system is in steady state so after sc study load flow study is performed, after that P.S goes to dynamic condⁿ so stability after that system is in steady state so again load flow analysis.
 - To limit the value of I_{sc}
 - (a) Series Resistance is not considered due to continuous process.
 - (b) Series Capacitance is not considered due to breakdown of inslⁿ.
 - (c) during the time of short circuit.
 - (d) Series reactors are widely used for limiting short ckt current. (to avoid saturation no core or air core reactor).
 - Resistance is a linear element until temp maintained const.
 - * $L = \frac{N\phi}{I}$ If then B^2 for high current saturation occurs. So after saturation $L \downarrow$. i.e.
 - * so inductor is a linear element until saturation takes place and capacitor is a linear element until voltage its final value.
 - Q.) A 100 kVA equipment has 5% impedance to limit the short ckt kVA to 250. the percentage reactance required for series reactor is? $\left(\frac{KVA}{KVA} \right)_{pu} = \frac{250}{100} \cdot 2.5$
- $I_{sc} (pu) = \frac{KVA_{pu} \cdot 250}{V_{pu} \cdot 100} = 2.5 pu$
- $I_{sc} (pu) = \frac{250}{100} \cdot 2.5 = 2.5 pu$
- $\frac{V(pu)}{X_{se} + jX} = 2.5 \Rightarrow \frac{1}{X_{se} + 0.05} = 2.5 \Rightarrow X_{se} + 0.05 = \frac{1}{2.5} = 0.4$
- $\Rightarrow X_{se} = 0.4 - 0.05 = 0.35$
- $X_{se} = 35\%$

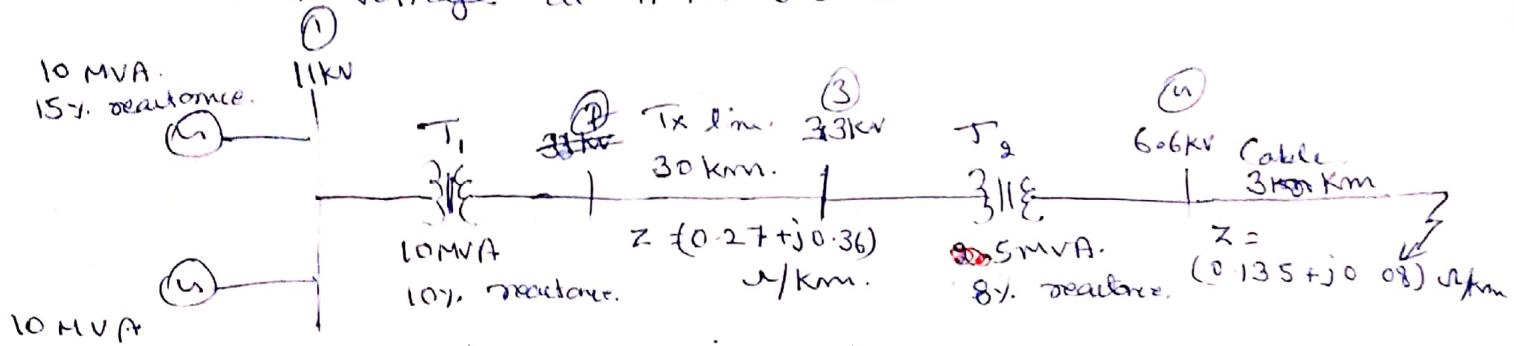For the radial m/s shown in fig (Q5), a three-phase fault occurs at F. Determine the fault current and the line voltage at 11 kV bus under fault conditions.



$$\text{Soln:} \quad \text{Base, MVA} = 100 \text{ MVA.}$$

$$X_b = \frac{(kV)^2}{\text{MVA}}, X_{pu} = \frac{X_b \text{ MVA}}{kV^2}$$

$$X_{G_1} = 10.15 \times \left(\frac{kV_{old}}{kV_{new}} \right)^2 \times \left(\frac{\text{MVA}_{new}}{\text{MVA}_{old}} \right) = 10.15 \times \left(\frac{11}{11} \right)^2 \times \frac{100}{10} = 10.15 \text{ pu.}$$

$$X_{G_2} = 10.125 \times \frac{100}{10} = 10.125 \text{ pu.} \quad X_{T_x} = \frac{Z \text{ (pu)}}{kV^2/\text{MVA}}$$



$$X_{T_1} = 10.01 \times \frac{100}{10} = 10.0 \text{ pu.}$$

$$X_{T_2} = 10.08 \times \frac{100}{5} = 10.8 \text{ pu.}$$

$$= \frac{30 \times (0.27 + j0.36)}{33^2 / 100}$$

$$= 0.744 + j0.99 \text{ pu}$$
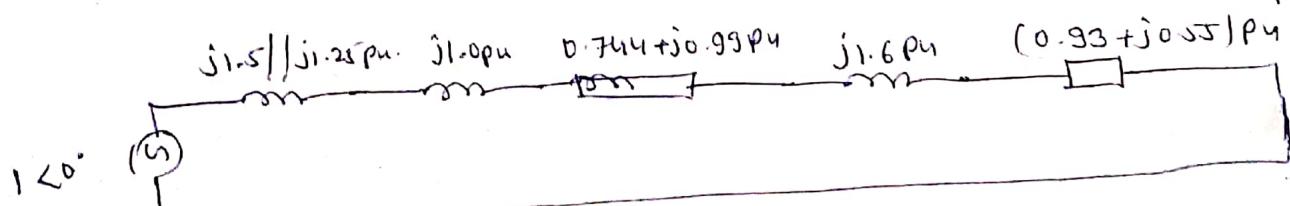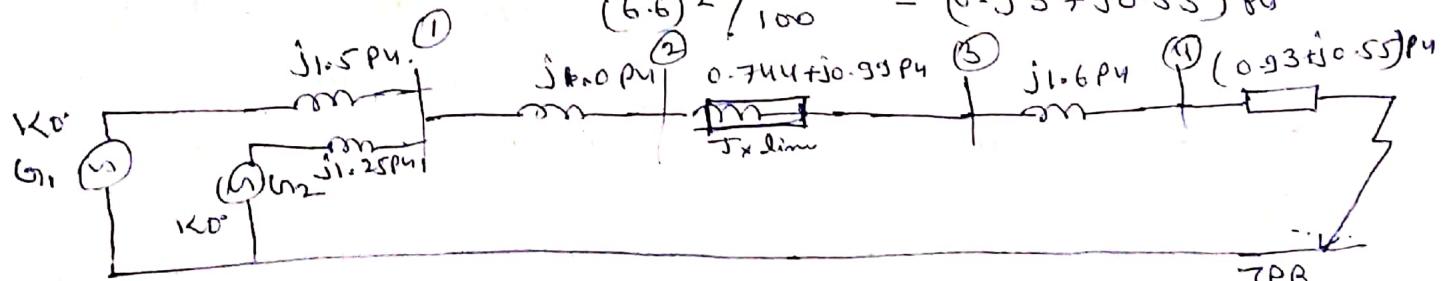
$$X_{\text{cable}} = \frac{3 \times (0.135 + j0.08)}{(6.6)^2 / 100} = (0.93 + j0.55) \text{ pu}$$



$$j1.5 || j1.25 \text{ pu.} = \frac{j1.5 \times j1.25}{j1.5 + j1.25} = j0.682.$$

$$\text{Total impedance.} = (j0.682 + j1.0 + j0.99 + j1.6 + j0.55) + (0.744 + 0.99)$$

$$= 1.67 \text{ u} + j4.82 \text{ u} = 5.1 < 70.8^\circ \text{ pu.}$$

$$I_{sc} = \frac{110}{5.1 < 70.8^\circ} = 0.196 < -70.8^\circ \text{ pu.}$$

$$I_{\text{Base}} = \frac{100 \times 10^3}{\sqrt{3} \times 6.6} = \frac{100 \times 10^3}{\sqrt{3} \times 6.6} = 8748$$

$$I_{SC} = 0.196 \times 8748 = 1714.61 \text{ A} \\ 1715 \text{ A.}$$

total impedance b/w F and 11 KV bus.

$$= 0.93 + j0.55 + (0.746 + j0.59) + j1.6 + 0.93 + j0.55 \\ = 1.674 + j4.14 = 4.43 \angle 76.8^\circ \text{ pu.}$$


$$\text{Voltage at } 11 \text{ KV bus} = 4.43 \angle 76.8^\circ \times 0.196 \angle -70.8^\circ \\ = 0.88 \angle -3^\circ \text{ pu.} = 0.88 \times 11 = 9.68 \text{ KV.}$$

Now a 100 MVA power generation with 11 KV bus is connected

→ x_L (leakage reactance in alternator) → In an ac mle any flux setup by load current which does not contribute to the useful flux of the mle is called a leakage flux. the effect of this leakage flux is to setup self induced emf in the armature wdg. which taken into account by introduction of leakage reactance drops. current voltage induce in the phases by leakage flux are the leakage reactance drops and lead the currents producing them by 90° degree.

→ This leakage flux makes the armature wdg inductive in nature. So wdg posses a leakage reactance in addition to the resistance. called synchronous reactance. $X_s = x_L + x_a$.

→ DC-offset in fault currents.

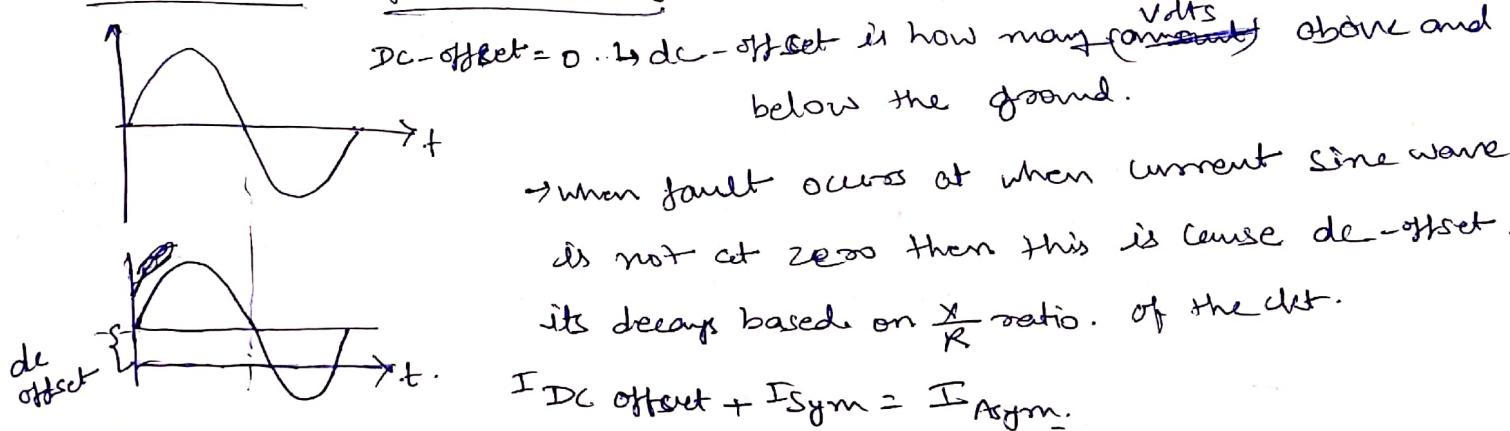

→ The initial value of the dc component is dependent on the exact time within a cycle at which the fault takes place. and the value of current at that time.

→ At the initiation of a fault, the current in any system can't instantly change (inductance opposes instant change) from its value of fault inception to that of its steady state value. To compensate for this, a dc comp is introduced. The dc component is equal to the value of the instantaneous ac current at fault inception and of opposite polarity.

→ mag of the dc component is dependent on where in the cycle the fault inception takes place.

in worse case, the initial dc-offset will be $\sqrt{2}$ times the symmetrical short ckt value (RMS).

$$I_{dc\text{-offset}} = \sqrt{2} I_k e^{-t/T} \rightarrow \text{completely decay after few cycles.}$$

I_k → Sym SC current.

$$T \rightarrow \text{decay time const} = \frac{1}{2\pi f} \left(\frac{x}{R} \right).$$

$t \rightarrow$ time since fault inception (ω)

→ For most distribution cB., a system time const of dc decay of 45 ms. (x/R of 17 at 60Hz) is assumed.

→ $\frac{x}{R} \uparrow$, ~~time~~ $T \uparrow$ so decay slower.

→ gen ckt typically larger $\frac{x}{R}$ ratio so 43 manufactured for this type of application would typically be designed for a system time const of 133 ms ($\frac{x}{R} = 50$ at 60Hz).

Assignment - I (8th sem)
Power System Design

Due Date:
9/04/2020

- Q. ① Write down the steps for symmetrical fault calculations.
- Q. ② A 3-phase, 20 MVA, 100 kV alternator has internal reactance of 5%. and negligible resistance. Find the external reactance per phase to be connected in series with the alternator so that steady current on short-ckt does not exceed 8 times the full load current.

Assignment - II (PSD) 8th sem

Due Date:
10/04/2020

- Q. ① List the types of faults occurs in P.S.
- Q. ② A 3-phase, 11 kV, ~~25~~ MVA generator with $X_0 = 0.05 \text{ pu}$, $X_1 = 0.2 \text{ pu}$, and $X_2 = 0.2 \text{ pu}$ is grounded through a reactance of 0.3Ω . Calculate the fault current for a single line to ground fault.
- Q. ③ Write short notes on
① Positive sequence n/w.
② Negative sequence n/w.